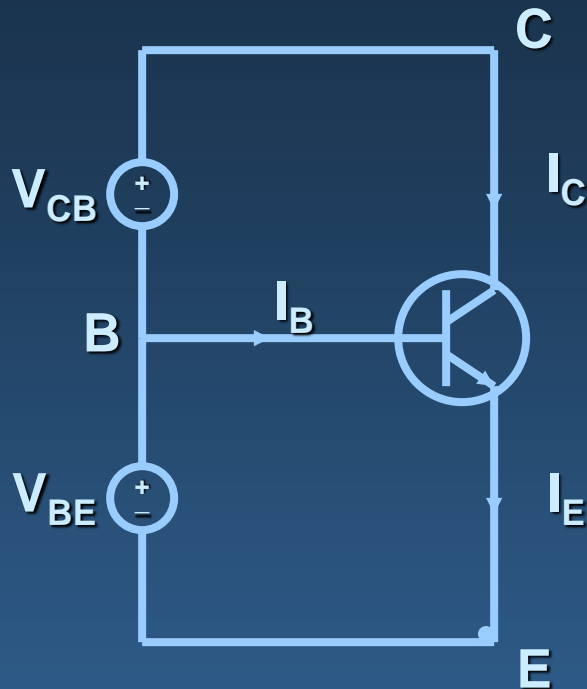




BJT Example

Using Common-Base NPN Circuit Configuration



Given: $I_B = 50 \mu\text{A}$, $I_C = 1 \text{ mA}$

Find: I_E , β , and α

Solution:

$$I_E = I_B + I_C = 0.05 \text{ mA} + 1 \text{ mA} = 1.05 \text{ mA}$$

$$\beta = I_C / I_B = 1 \text{ mA} / 0.05 \text{ mA} = 20$$

$$\alpha = I_C / I_E = 1 \text{ mA} / 1.05 \text{ mA} = 0.95238$$


α could also be calculated using the value of β with the formula from the previous slide.

$$\alpha = \frac{\beta}{\beta + 1} = \frac{20}{21} = 0.95238$$



BJT Transconductance Curve

Typical NPN Transistor ¹

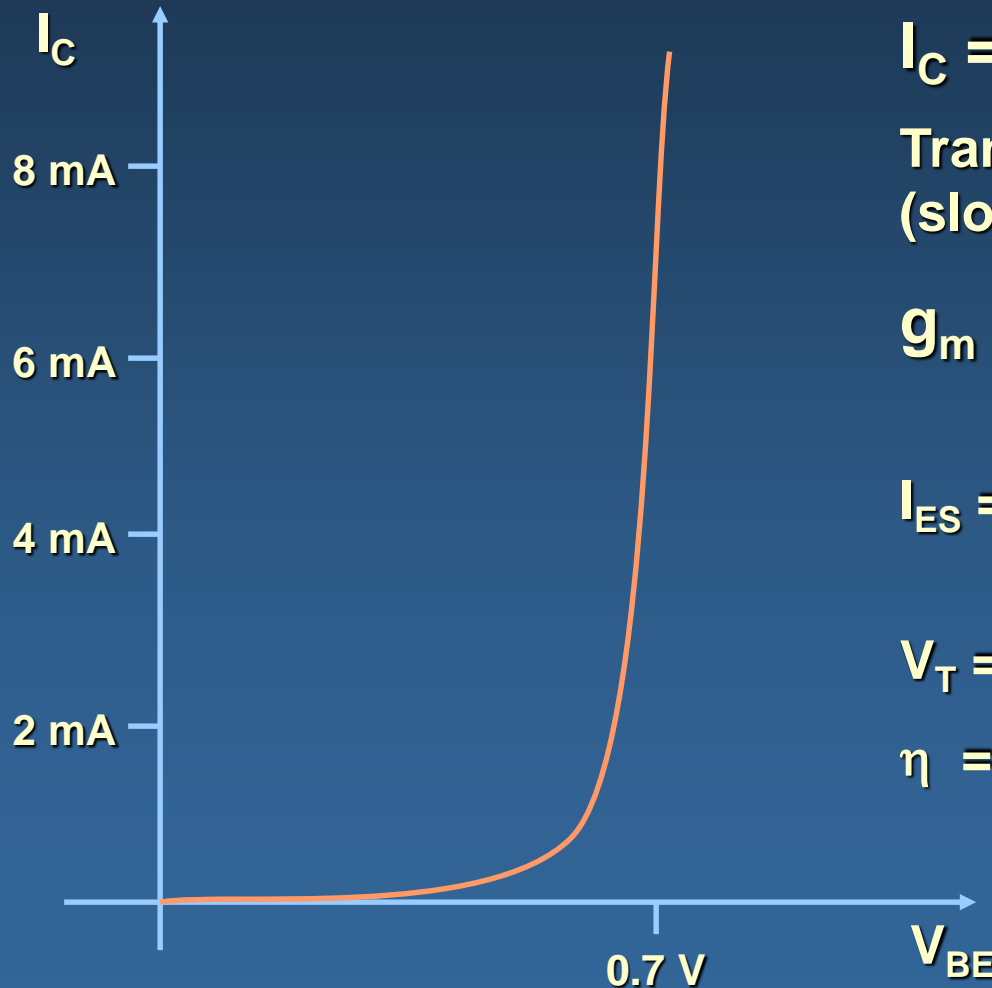

Collector Current:

$$I_C = \alpha I_{ES} e^{V_{BE}/\eta V_T}$$

Transconductance:
(slope of the curve)

$$g_m = \frac{\partial I_C}{\partial V_{BE}}$$

I_{ES} = The reverse saturation current
of the B-E Junction.

$$V_T = kT/q = 26 \text{ mV (@ } T=300\text{K)}$$

η = the emission coefficient and is
usually ~ 1



Modes of Operation

Active:

- Most important mode of operation
- Central to amplifier operation
- The region where current curves are practically flat

Saturation:

- Barrier potential of the junctions cancel each other out causing a virtual short

Cutoff:

- Current reduced to zero
- Ideal transistor behaves like an open switch

* Note: There is also a mode of operation called inverse active, but it is rarely used.



Three Types of BJT Biasing

Biasing the transistor refers to applying voltage to get the transistor to achieve certain operating conditions.

Common-Base Biasing (CB) : input = V_{EB} & I_E
output = V_{CB} & I_C

Common-Emitter Biasing (CE): input = V_{BE} & I_B
output = V_{CE} & I_C

Common-Collector Biasing (CC): input = V_{BC} & I_B
output = V_{EC} & I_E



Common-Base

Although the Common-Base configuration is not the most common biasing type, it is often helpful in the understanding of how the BJT works.

Emitter-Current Curves

