



# Common-Base

## Circuit Diagram: NPN Transistor




The Table Below lists assumptions that can be made for the attributes of the common-base biased circuit in the different regions of operation. Given for a Silicon NPN transistor.

Region of Operation	$I_C$	$V_{CE}$	$V_{BE}$	$V_{CB}$	C-B Bias	E-B Bias
Active	$\beta I_B$	$=V_{BE}+V_{CE}$	$\sim 0.7V$	$\bigcirc 0V$	Rev.	Fwd.
Saturation	Max	$\sim 0V$	$\sim 0.7V$	$-0.7V < V_{CE} < 0$	Fwd.	Fwd.
Cutoff	$\sim 0$	$=V_{BE}+V_{CE}$	$\odot 0V$	$\bigcirc 0V$	Rev.	None /Rev.




# Common-Emitter

## Circuit Diagram

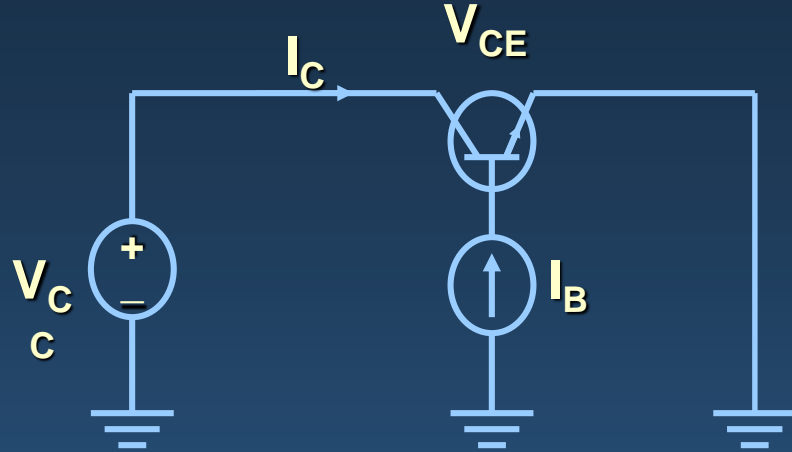

## Collector-Current Curves

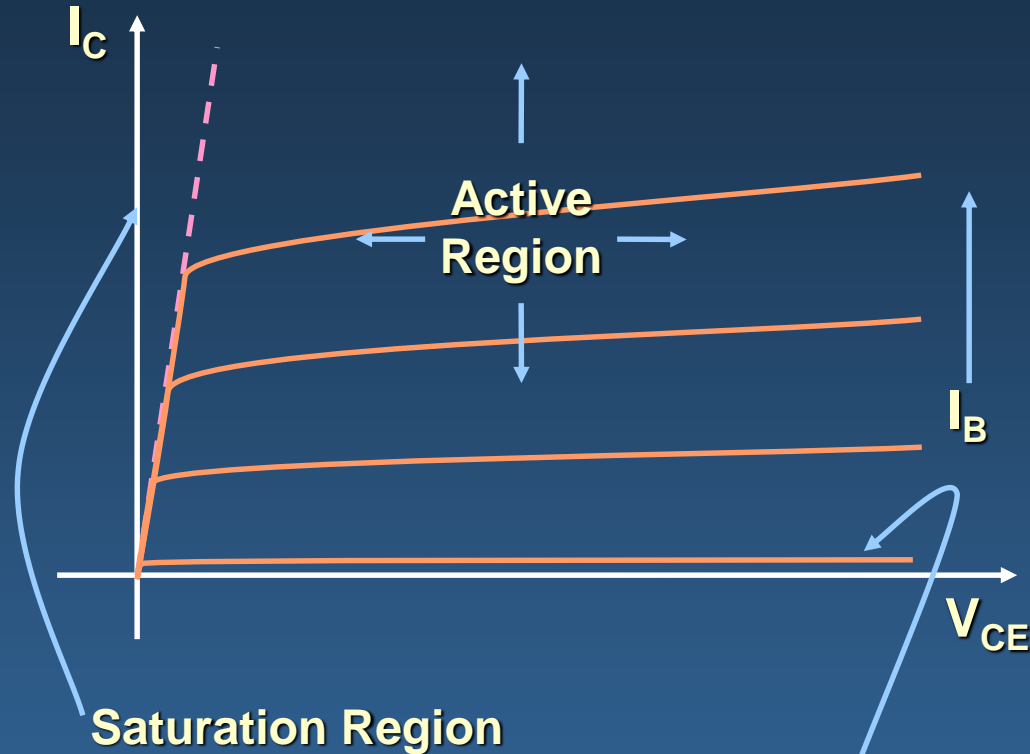

**Cutoff Region**  
 $I_B = 0$

Region of Operation	Description
Active	Small base current controls a large collector current
Saturation	$V_{CE(sat)} \sim 0.2V$ , $V_{CE}$ increases with $I_C$
Cutoff	Achieved by reducing $I_B$ to 0, Ideally, $I_C$ will also equal 0.




# Common-Collector
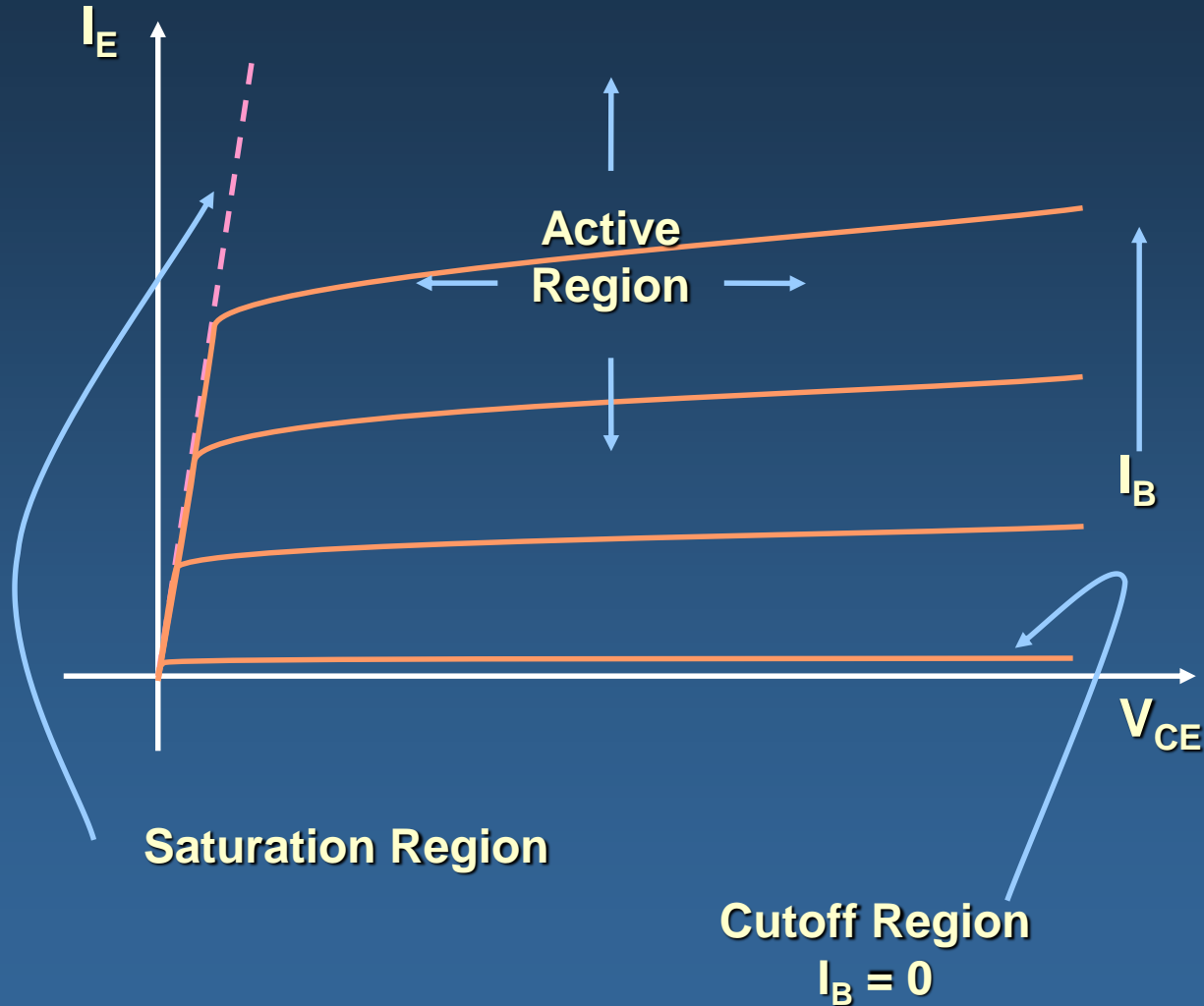
## Emitter-Current Curves

The Common-Collector biasing circuit is basically equivalent to the common-emitter biased circuit except instead of looking at  $I_C$  as a function of  $V_{CE}$  and  $I_B$  we are looking at  $I_E$ .


Also, since  $\alpha \sim 1$ , and  $\alpha = I_C/I_E$  that means  $I_C \sim I_E$




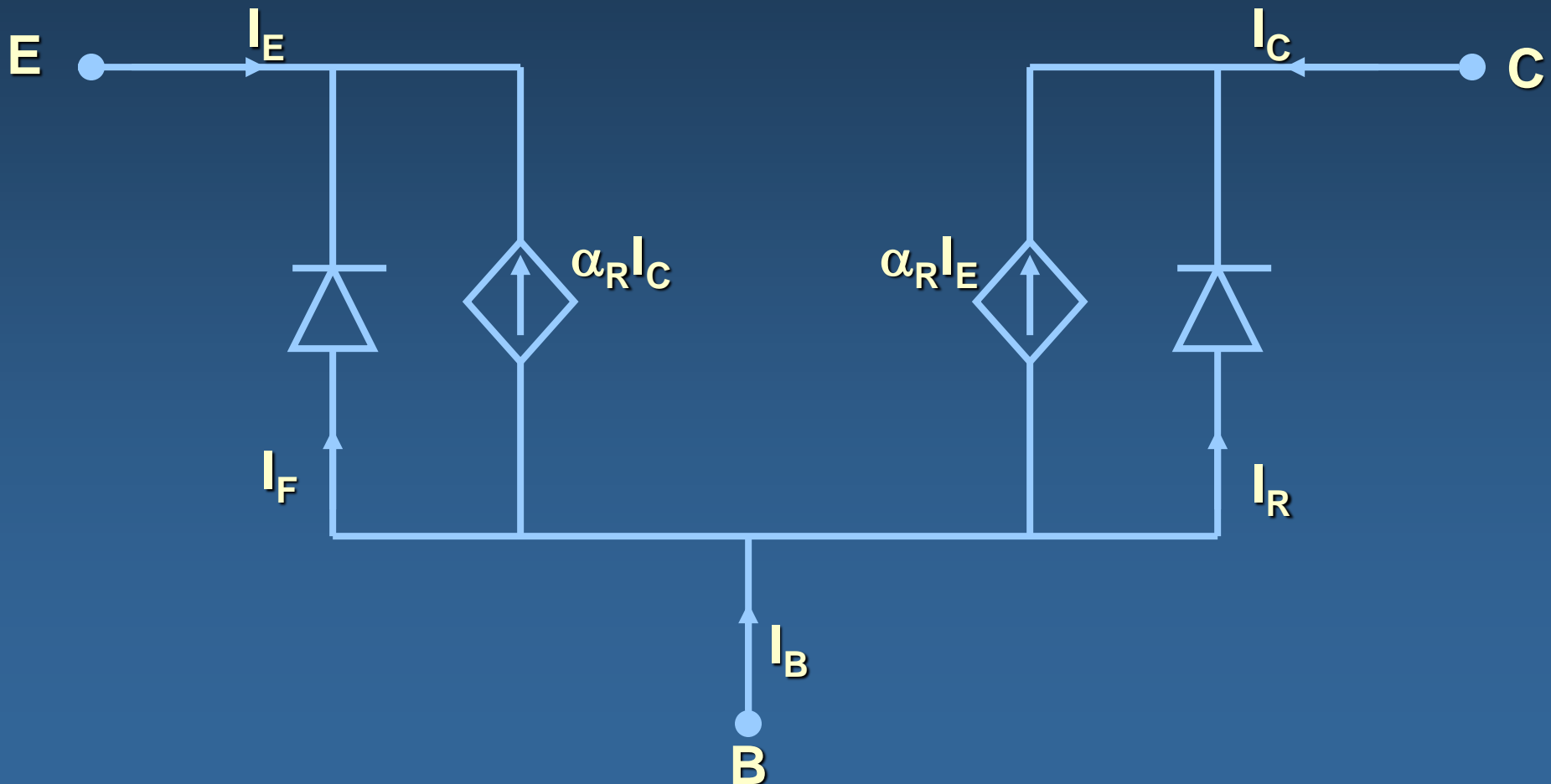
# Eber-Moll BJT Model

The Eber-Moll Model for BJTs is fairly complex, but it is valid in all regions of BJT operation. The circuit diagram below shows all the components of the Eber-Moll Model:





# Eber-Moll BJT Model

$\alpha_R$  = Common-base current gain (in forward active mode)

$\alpha_F$  = Common-base current gain (in inverse active mode)

$I_{ES}$  = Reverse-Saturation Current of B-E Junction

$I_{CS}$  = Reverse-Saturation Current of B-C Junction

$$I_C = \alpha_F I_F - I_R \quad I_B = I_E - I_C$$

$$I_E = I_F - \alpha_R I_R$$

$$I_F = I_{ES} [\exp(qV_{BE}/kT) - 1] \quad I_R = I_{CS} [\exp(qV_{BC}/kT) - 1]$$

- ★ If  $I_{ES}$  &  $I_{CS}$  are not given, they can be determined using various BJT parameters.