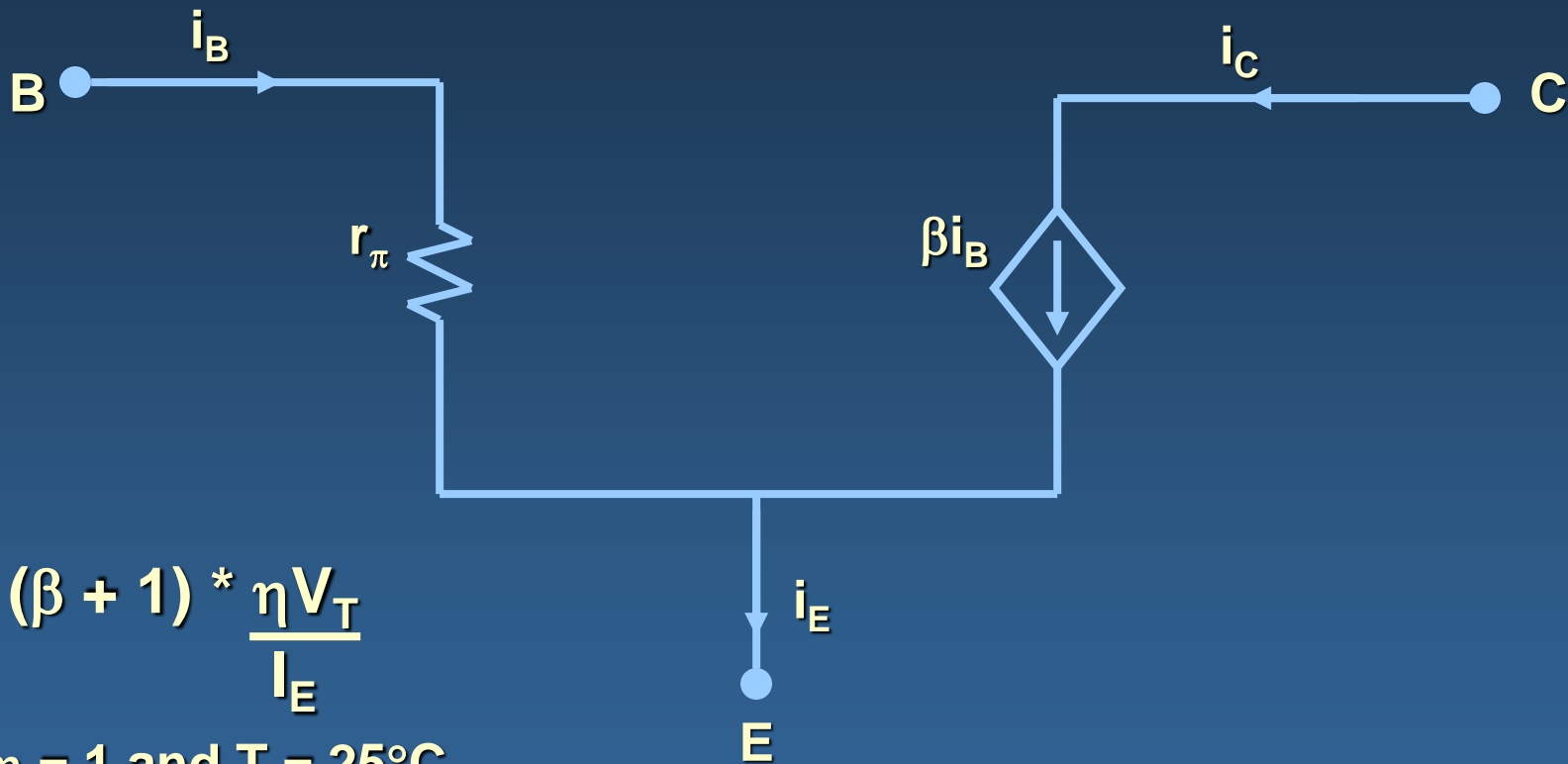




Small Signal BJT Equivalent Circuit

The small-signal model can be used when the BJT is in the active region.
The small-signal active-region model for a CB circuit is shown below:



$$r_{\pi} = (\beta + 1) * \frac{\eta V_T}{I_E}$$

@ $\eta = 1$ and $T = 25^{\circ}\text{C}$

$$r_{\pi} = (\beta + 1) * \frac{0.026}{I_E}$$


Recall:

$$\beta = I_C / I_B$$



The Early Effect (Early Voltage)

Note: Common-Emitter Configuration

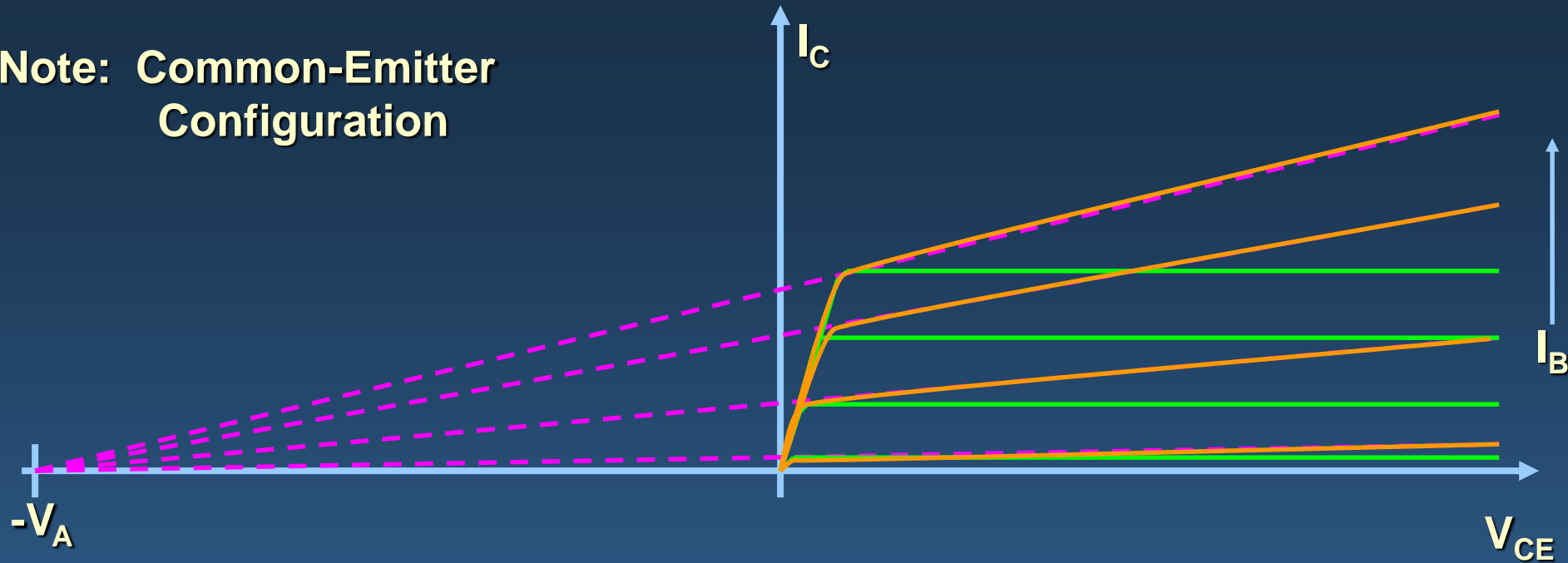

Green = Ideal I_C

Orange = Actual I_C (I_C')

$$I_C' = I_C \left(\frac{V_{CE} + 1}{V_A} \right)$$




Early Effect Example

Given: The common-emitter circuit below with $I_B = 25\mu\text{A}$,
 $V_{CC} = 15\text{V}$, $\beta = 100$ and $V_A = 80$.

Find: a) The ideal collector current
b) The actual collector current

Circuit Diagram

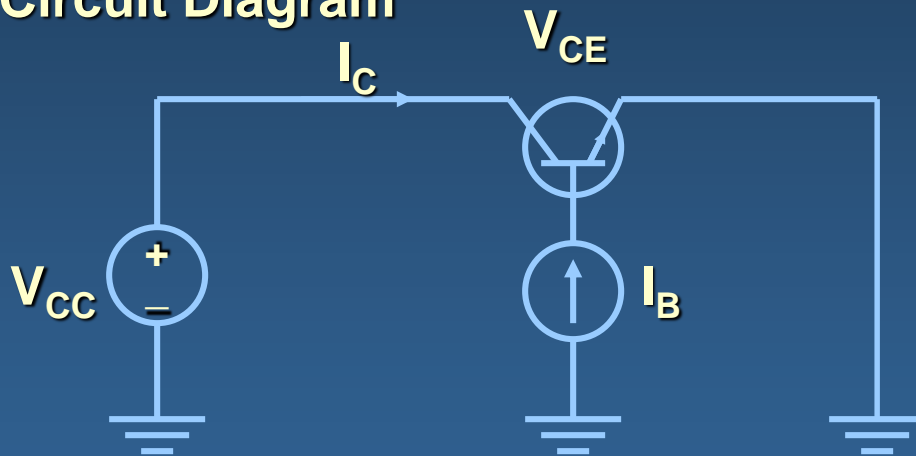

$$\beta = 100 = I_C / I_B$$

a)

$$I_C = 100 * I_B = 100 * (25 \times 10^{-6} \text{ A})$$

$$I_C = 2.5 \text{ mA}$$

$$\text{b) } I_C' = I_C \left(\frac{V_{CE} + 1}{V_A} \right) = 2.5 \times 10^{-3} \left(\frac{15 + 1}{80} \right) = 2.96 \text{ mA}$$

$$I_C' = 2.96 \text{ mA}$$

Breakdown Voltage

The maximum voltage that the BJT can withstand.

$BV_{CEO} =$ The breakdown voltage for a common-emitter biased circuit. This breakdown voltage usually ranges from ~20-1000 Volts.

$BV_{CBO} =$ The breakdown voltage for a common-base biased circuit. This breakdown voltage is usually much higher than BV_{CEO} and has a minimum value of ~60 Volts.

Breakdown Voltage is Determined By:

- The Base Width
- Material Being Used
- Doping Levels
- Biasing Voltage

