

# Power amplifiers - BJT

## Power amplifiers (1)

Fundamental function of this amplifier is to provide the **power levels** required to **drive the load**. Consequently the active devices in the power amplifiers must be able to **dissipate** the **thermal energy** produced, to contain the rise in temperature.

The temperature must not exceed the maximum value  $T_{JMax}$  (**maximum junction temperature**) characteristic value of each semiconductor device (provided in datasheet of each Trans.).

If the junction temperature exceeds this maximum value, usually between  $150 \div 200$  ° C, the device is destroyed. Therefore in general the fundamental requirements of such devices are:

High geometric **dimensions**.

Realization in **distinct element**.

**Metal Case** to help heat dissipation.

**Collector** (where it is dissipated more heat) mounted on the case.



Typical case called TO3 for power devices. The cylinder diameter is 2.2 cm. The lower plate is approximately 4 cm wide and has two holes to allow the connection to a heat sink.

## Power amplifiers (2)

This amplifier is typically the last stage, or the **output stage** of an amplifier system. The previous stage can be designed to realize: the necessary **voltage amplification**, **buffer** or to change the characteristics of the signal.

To supply the **maximum power** at a generic load, **maximum current and voltage variation** must be ensured


These conditions imply essentially that:

- the device must work over the **whole range** of its output characteristics,
- that the **working point** must be chosen appropriately.

The device works with great signals and fundamental consequences are:

Small-signal models and the linear analysis are not valid, the distortion of the signal is not negligible.

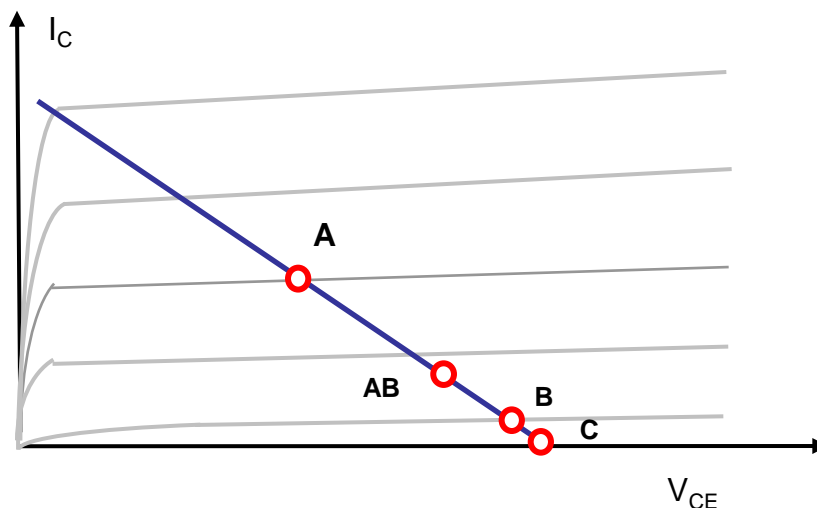The power amplifiers can be **classified** taking into account the **biasing** and consequently the **period part** in which the transistor is in conduction (in the presence of an input signal).




## Power amplifiers (3)

**Class A Amplifier:** the working point is located at the **center** of characteristics, consequently applying a sinusoidal input signal, the device is in conduction over the entire period.

**Class B Amplifier:** the working point is placed in **interdiction**, so that the current and the power absorbed by the device in the absence of signal are zero. Given a sinusoidal input signal, the device is in conduction on half period.



**Class AB amplifier:** it is midway between the Class A and the Class B.

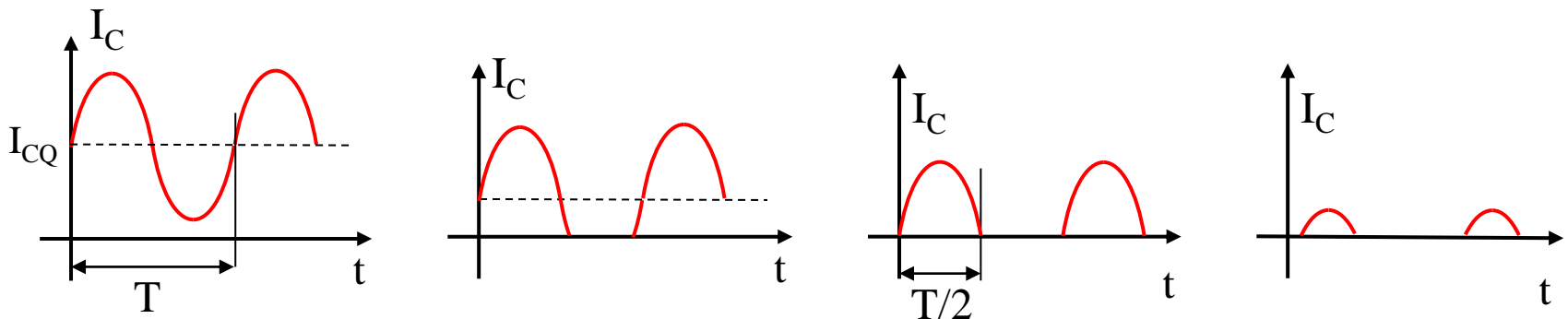**Amplifier Class C:** the working point is placed so that the device is in conduction only for less than half the period of the sinusoidal signal injected at the input.





# Power amplifiers (4)

## Class A Amplifier

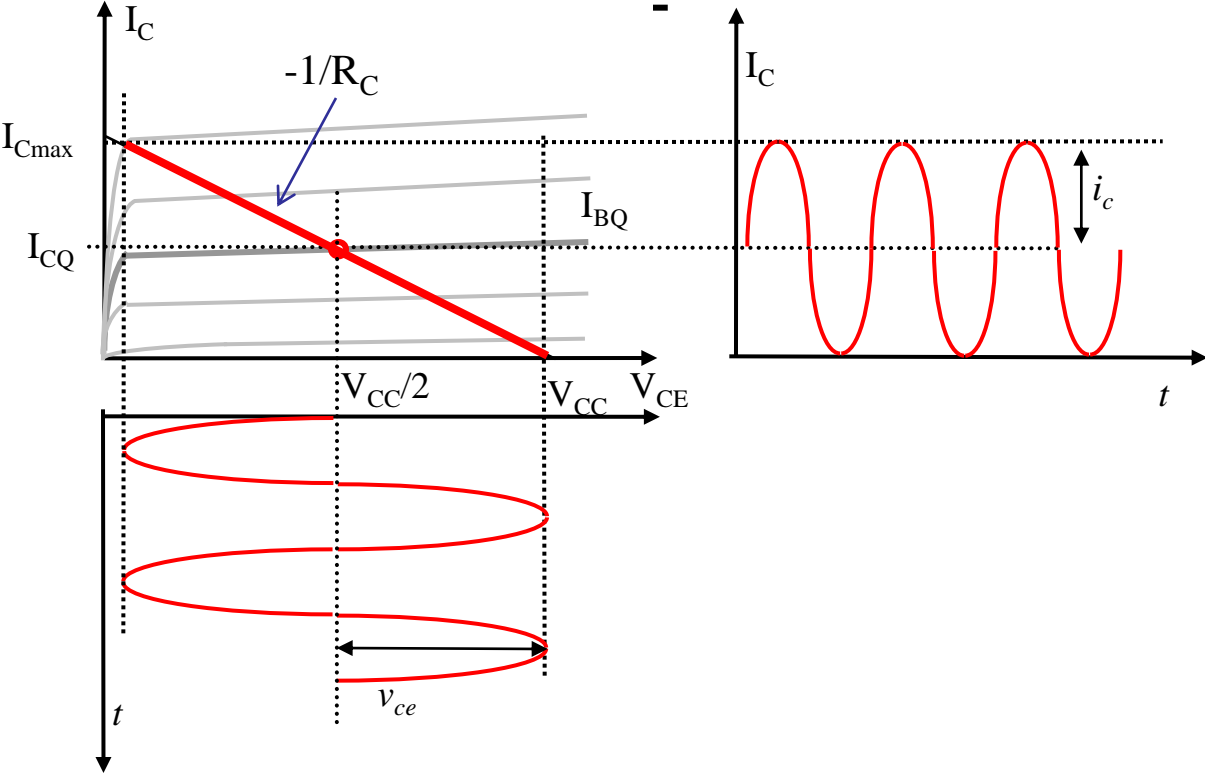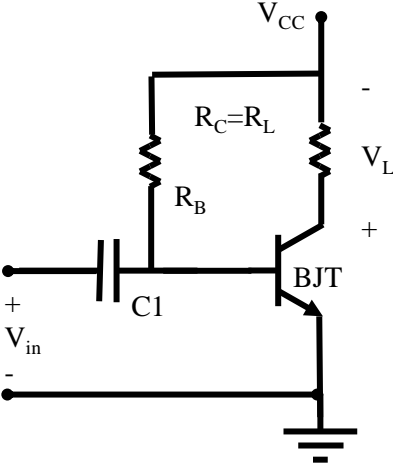







# Power amplifiers (5)

## Class A Amplifier

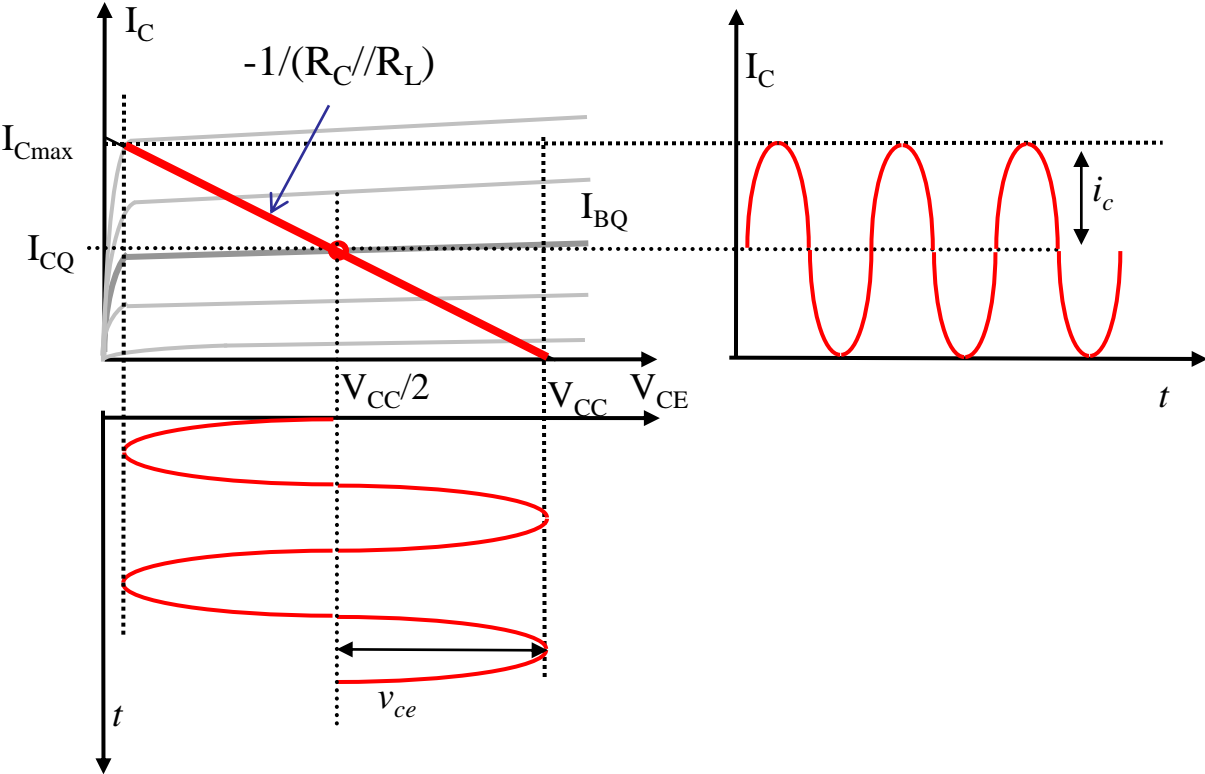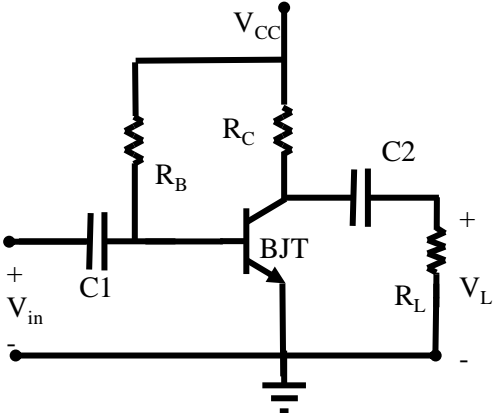

# Power amplifiers (6)

## Class B Amplifier

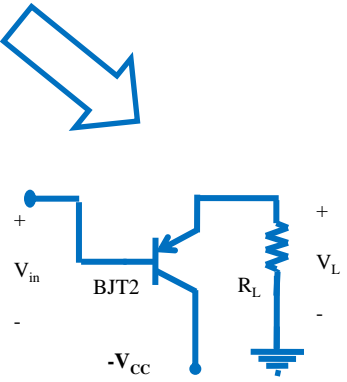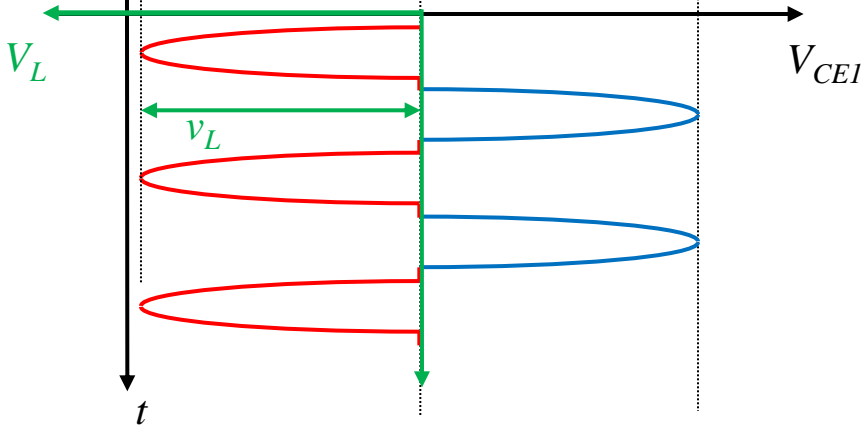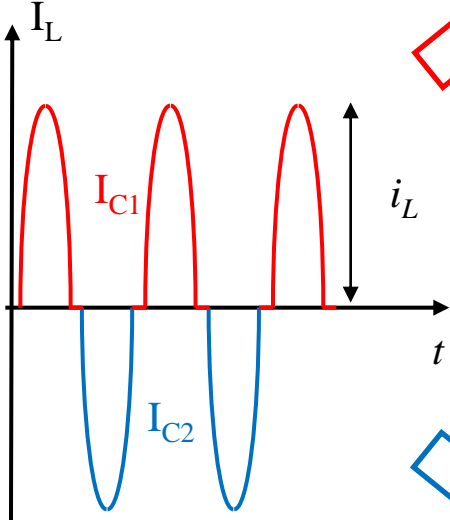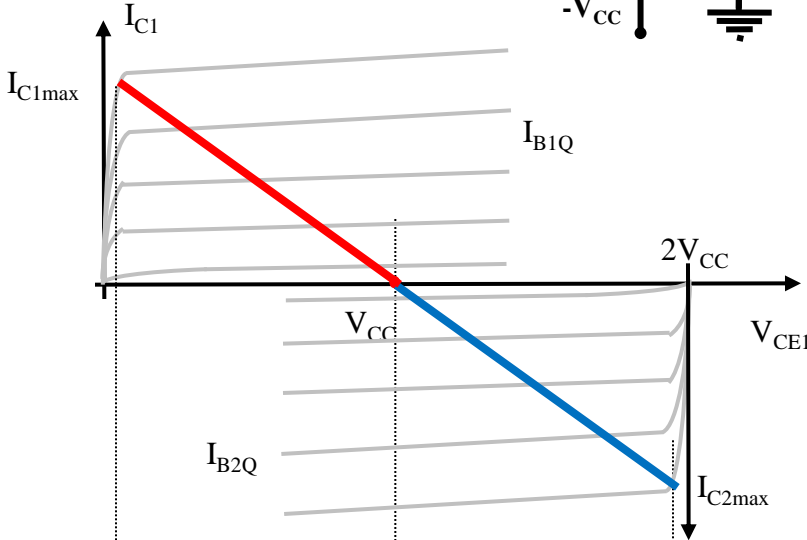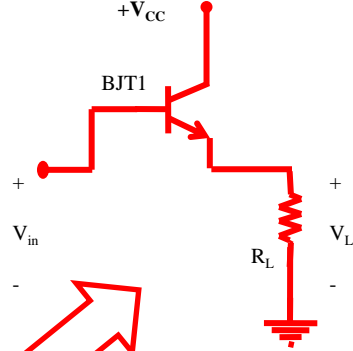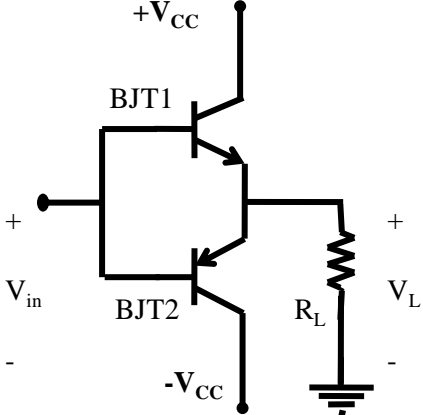

## Power amplifiers (6)

Some basic parameters of the power amplifier are:

$$G = \frac{P_L}{P_{in}} = \text{Power gain}$$

$$\eta = \frac{P_L}{P_{dc}} = \text{Efficiency}$$

Where:

$P_L$  is the load power,

$P_{in}$  is the input power

$P_{dc}$  is the supply power.

Class A where the load is crossed by the bias current → maximum  $\eta = 25\%$

Class A where the load is not crossed by the bias current → maximum  $\eta = 50\%$



Classe B → maximum  $\eta = 78\%$



# Power amplifiers (7)
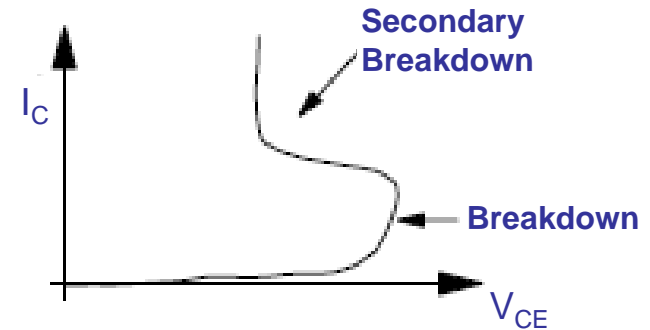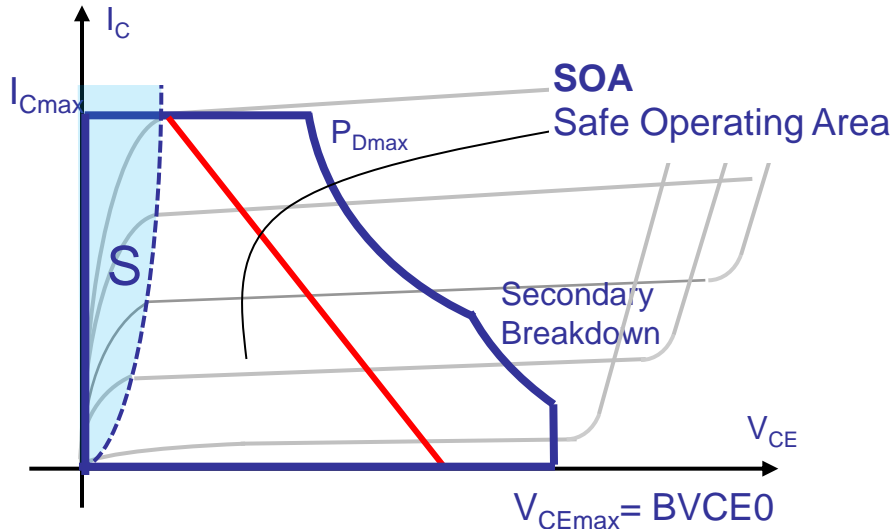
## Safe Operating Area

Power devices there are **limits** in which the device can work. These are represented on the characteristics of the device by means of an area in which the load curve must be contained



**Voltage limit** →  $V_{CEmax}$ , it is due to the **voltage breakdown** (BVCE0) of the junction BC.

**Current limit** →  $I_{Cmax}$ , current which **melts the connections** between leads and semiconductor.

**Dissipated power limit** →  $P_{Dmax}$

**Secondary breakdown** → Due to the **non-uniform flow** of the base-emitter junction current, which causes localized power dissipation and temperature increase at certain points “hot spots”.

**Region S** → represents the **saturation region** which is normally avoided in linear applications since it is highly non-linear. However, digital circuits often make use of this part of the characteristic.

## Power amplifiers (7)

### Thermal resistance

Assuming a situation in which the transistor works in the air. The heat dissipated by the junction is transmitted to the device case then to the surrounding environment.


In conditions of **thermal equilibrium** in which the transistor dissipates power ( $P_D$ ), the **junction temperature** responds to the following relation:

$$T_j - T_A = \theta_{jA} P_D$$

$\theta_{jA}$  is called **thermal resistance** between junction and ambient and has unit of measurement °C/W. Using the equation above shows that:

- **junction temperature** increases with the dissipated power. Taking into account that in order not to destroy the transistor the  $T_j$  must not exceed  $T_{jMax}$  it is essential to work with low values of thermal resistance.
- The **maximum dissipated power** decreases with the increasing of  $T_A$ .

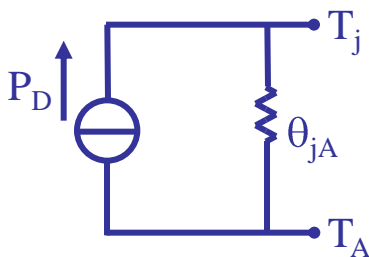The above relation can be expressed by an equivalent electric circuit:




## Power amplifiers (8)

### Maximum dissipated power

In general manufacturers, to describe the device ability to dissipate power, provide three types of data:

- The **maximum dissipated power**  $P_{D0}$  which is guaranteed for temperatures below  $T_0$ .
- The **maximum junction temperature**  $T_{JMax}$ .
- The **thermal resistance**, whose inverse is the **decrement factor** of the power dissipated for temperatures higher than  $T_0$

Examining the situation of an isolated transistor account must be taken of thermal resistance between junction and ambient ( $\theta_{jA}$ ) and the temperature to which it is guaranteed the power dissipated  $P_{D0A}$  (usually  $25^\circ\text{C}$ ). Therefore, the reduction of the maximum power dissipated is described by the curve shown in the figure and its value, for  $T_A > 25^\circ\text{C}$ , can be obtained from the equations below:




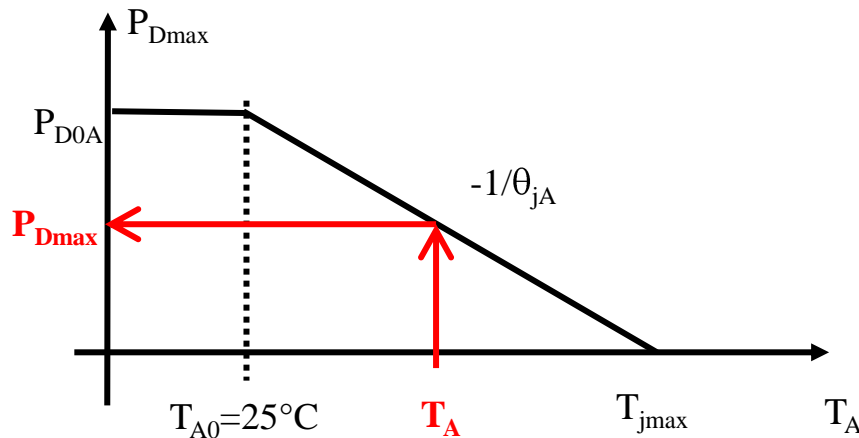


$$P_{Dmax} = \frac{T_{jmax} - T_A}{\theta_{jA}}$$


$$\theta_{jA} = \frac{T_{jmax} - T_{A0}}{P_{D0}}$$



# Power amplifiers (11)

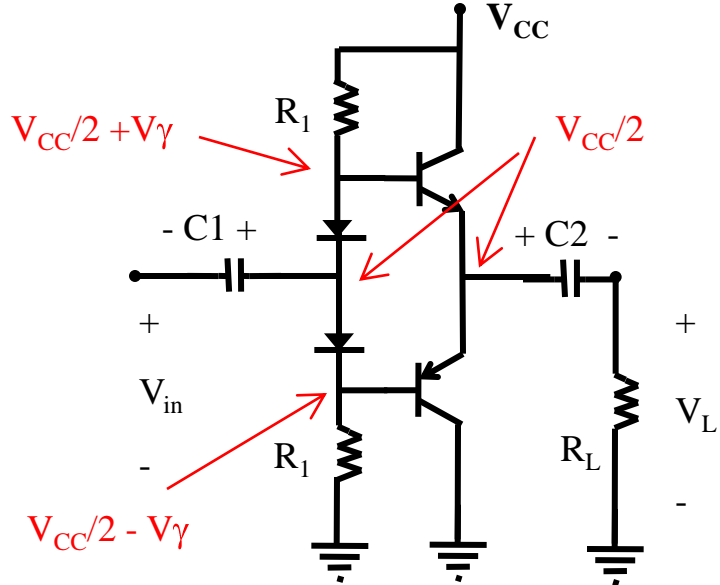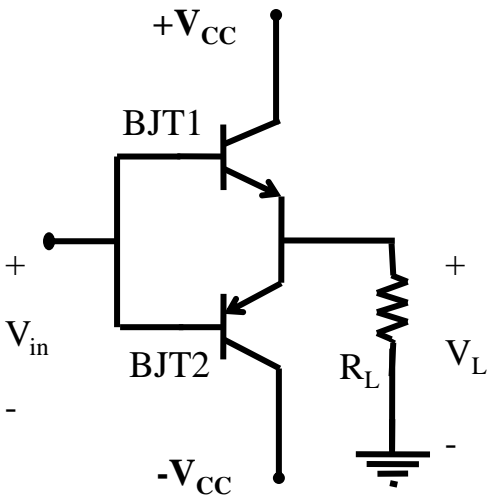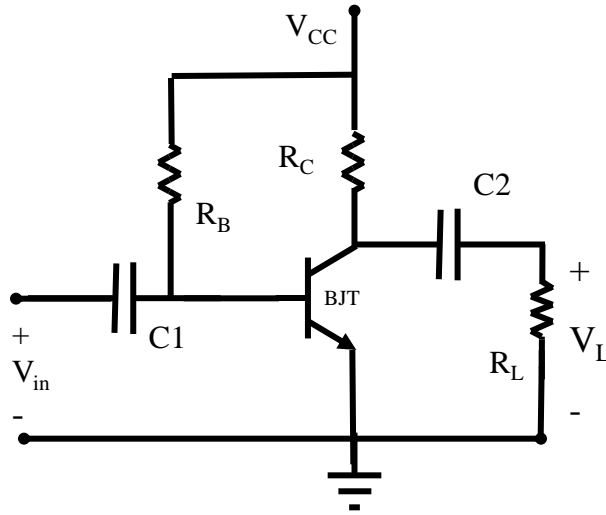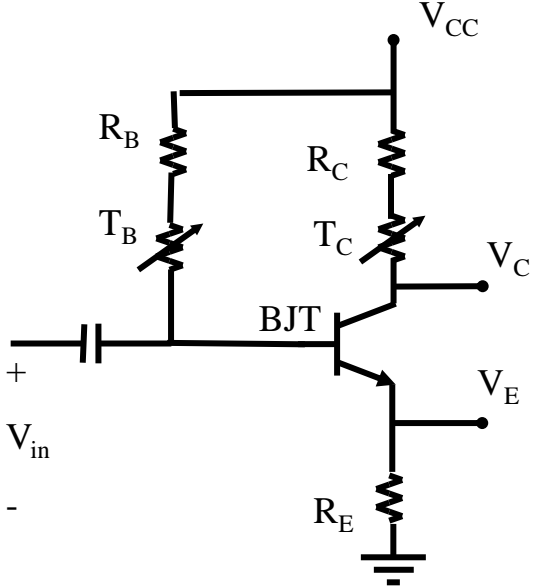

# Power amplifiers (12)

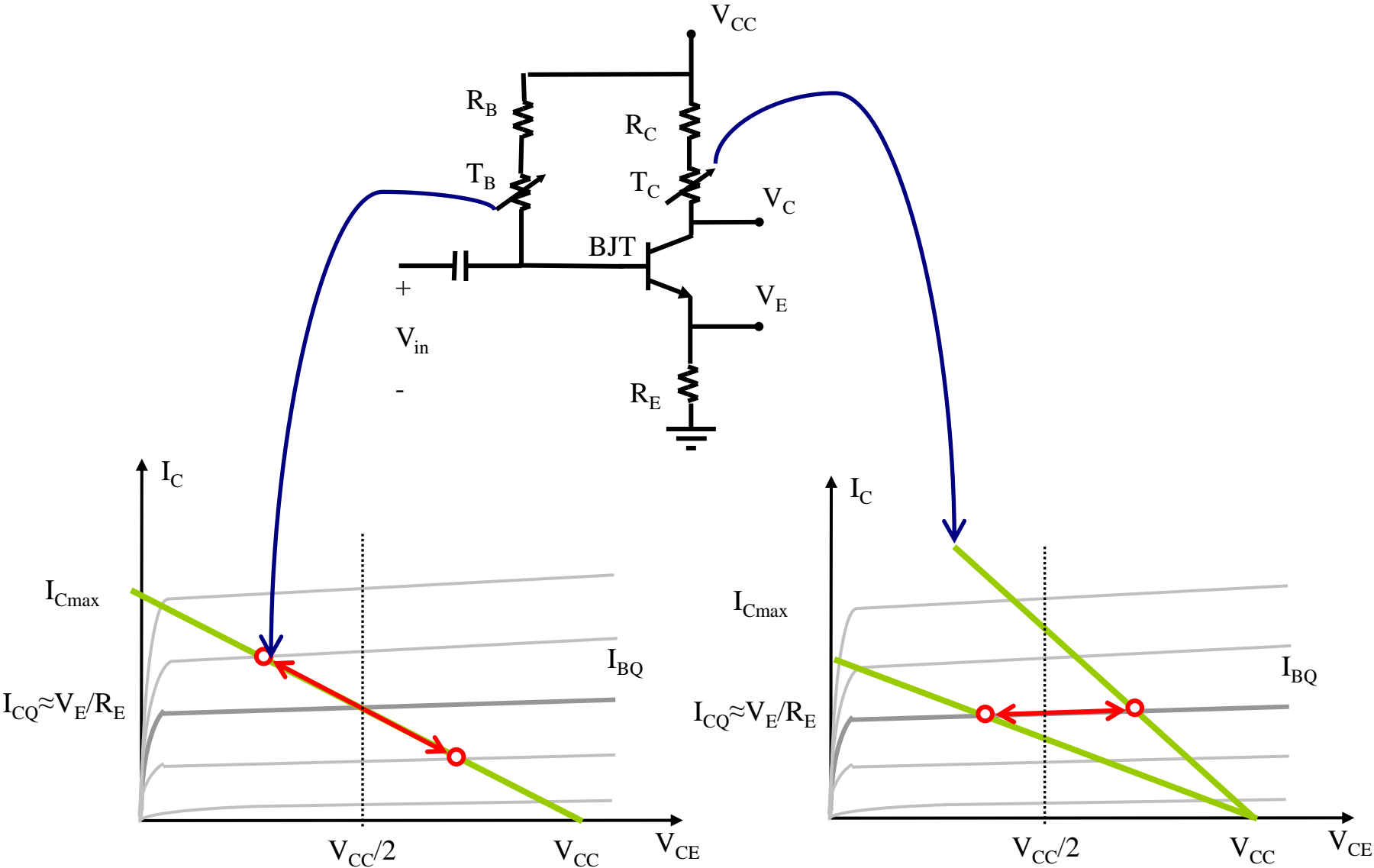


# Power amplifiers (13)

$R_1$  fixed to obtain a current  $I_{R1}$  equal to 1/10 of the average current on the BJTs.

$R_L$  fixed to maximize the output power.

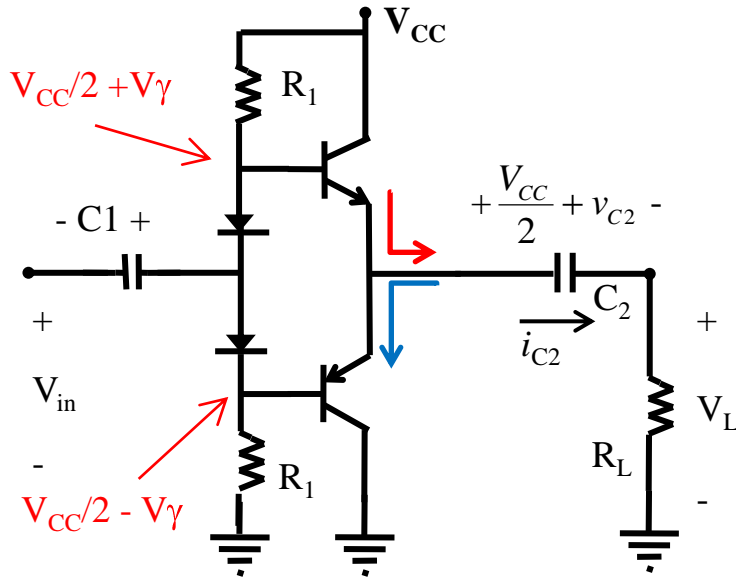$C_2$  chosen to obtain a voltage variation on  $C_2$  equal to  $V_{CC}/100$




$$2R_1 = \frac{V_{CC} - 2V_\gamma}{\frac{I_{C,Max}}{10\pi}}$$


$$R_L = \frac{V_{CC} - V_{CC}/2}{I_{C,Max}}$$

$$C_2 = \frac{100 \cdot I_{C,Max} \cdot T}{\pi \cdot V_{CC}}$$

$$I_C = \frac{\Delta Q}{\Delta T} = C_2 \frac{\Delta V_C}{\Delta T}$$
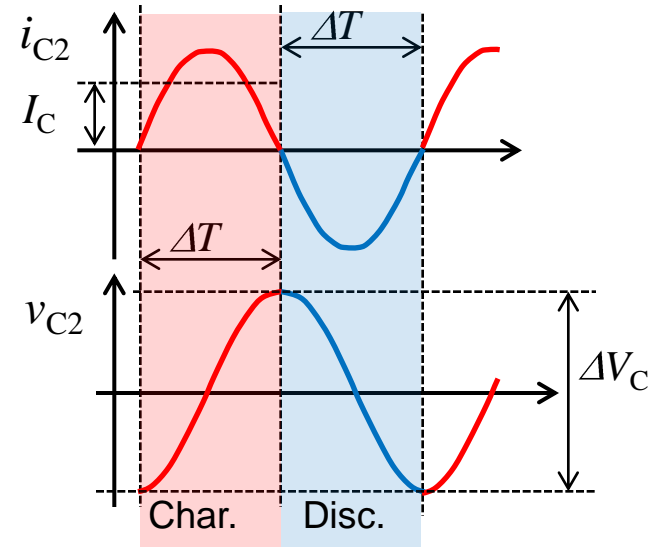
$$I_C = 2 \frac{I_{C,Max}}{\pi}; \quad \Delta V_C = \frac{V_{CC}}{100}; \quad \Delta T = \frac{T}{2} = \frac{1}{2f_{min}}$$



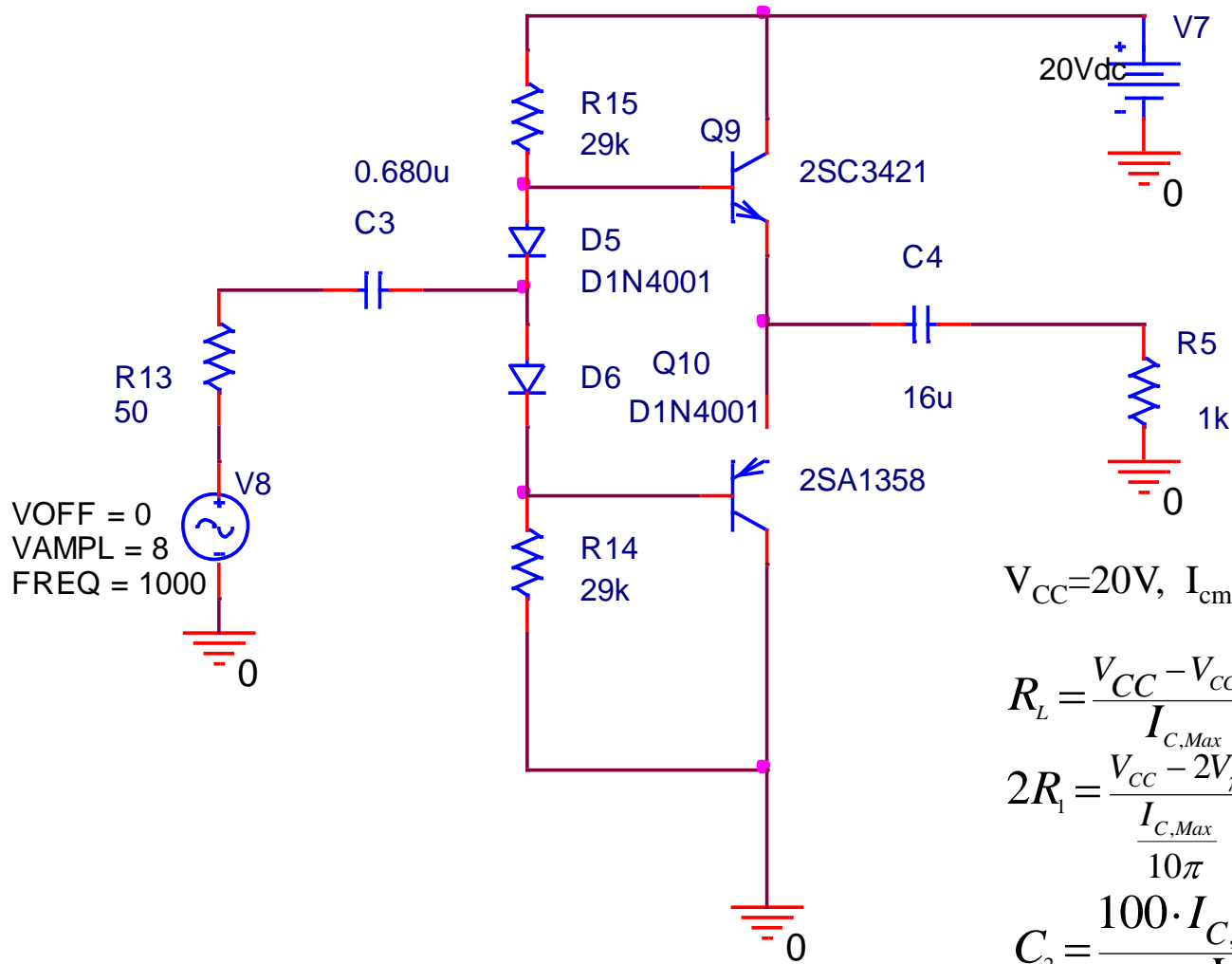


$V_{CC}=20V, I_{cmax}=10mA$

$$R_L = \frac{V_{CC} - V_{CC}/2}{I_{C,Max}} = 1K\Omega$$


$$2R_1 = \frac{V_{CC} - 2V_\gamma}{\frac{I_{C,Max}}{10\pi}} \approx 58.7K\Omega$$

$$C_2 = \frac{100 \cdot I_{C,Max} \cdot T}{\pi \cdot V_{CC}} \approx 16\mu F$$


$C_4=16\text{mF}$

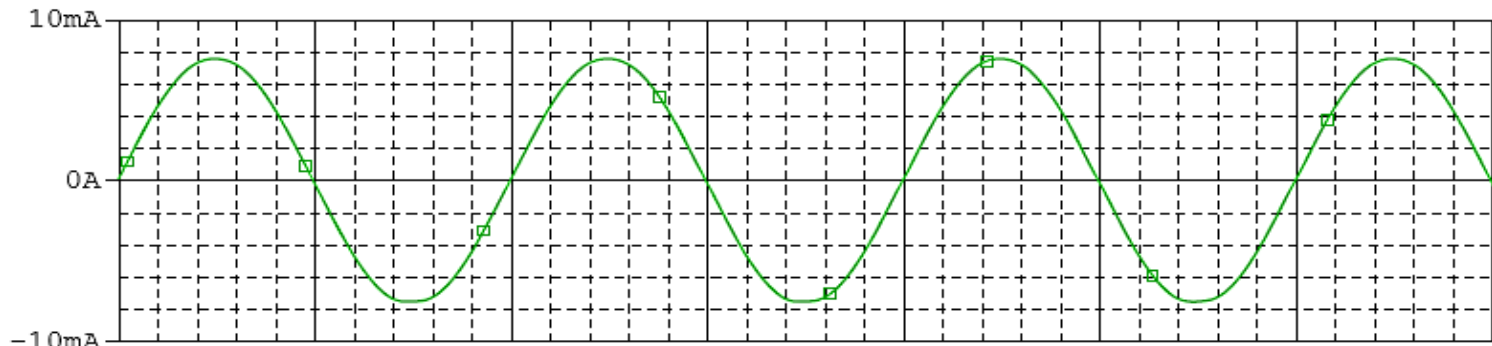

□ I (C4)

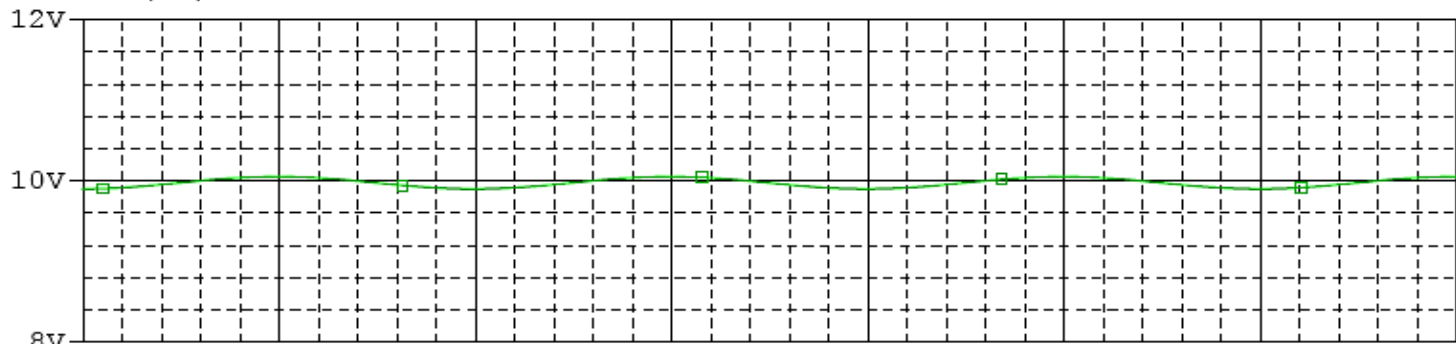

□ V (C4:1, C4:2)

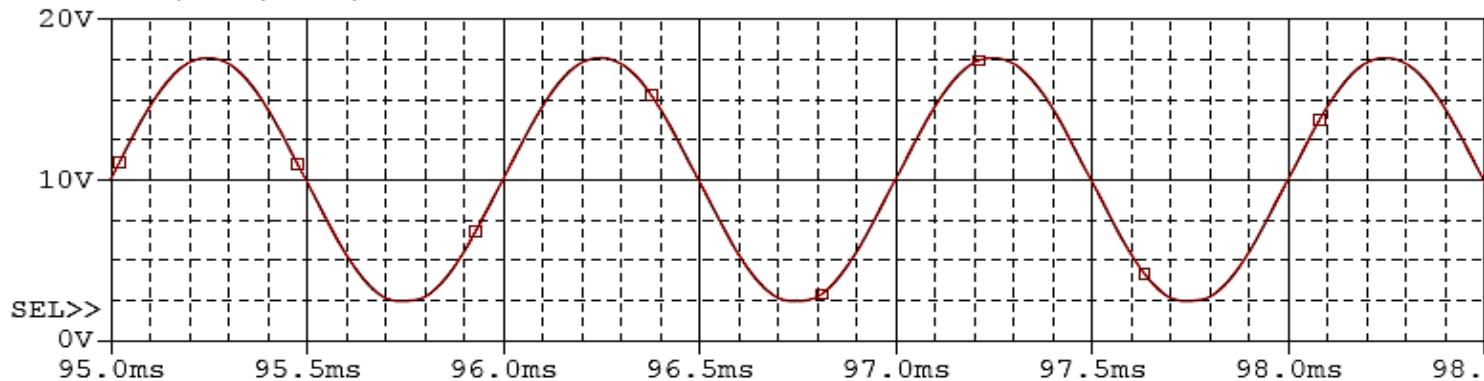

□ V (C4:1)

Time



$C_4=1.6\text{mF}$

