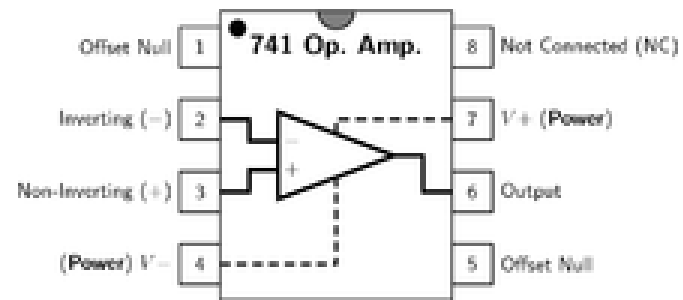


What is an Op-Amp? – The Surface

- An Operational Amplifier (Op-Amp) is an integrated circuit that uses external voltage to amplify the input through a very high gain.
- We recognize an Op-Amp as a mass-produced component found in countless electronics.



What an Op-Amp looks like to a lay-person




What an Op-Amp looks like to an engineer




What is an Op-Amp? – The Layout

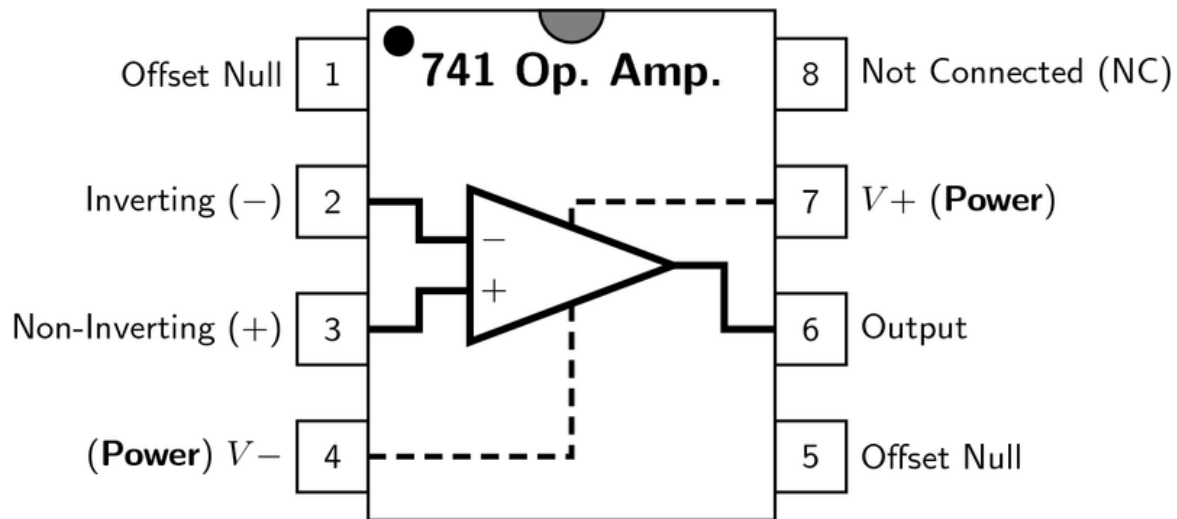- There are 8 pins in a common Op-Amp, like the 741 which is used in many instructional courses.




What is an Op-Amp? – The Inside

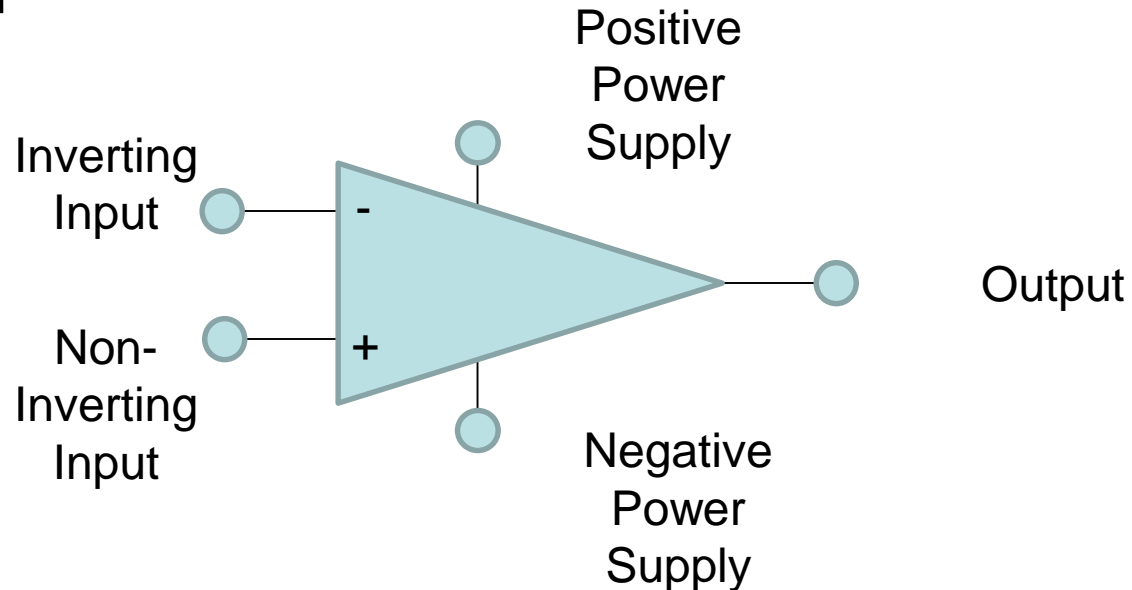- The actual count varies, but an Op-Amp contains several Transistors, Resistors, and a few Capacitors and Diodes.
- For simplicity, an Op-Amp is often depicted as this:



History of the Op-Amp – The Dawn

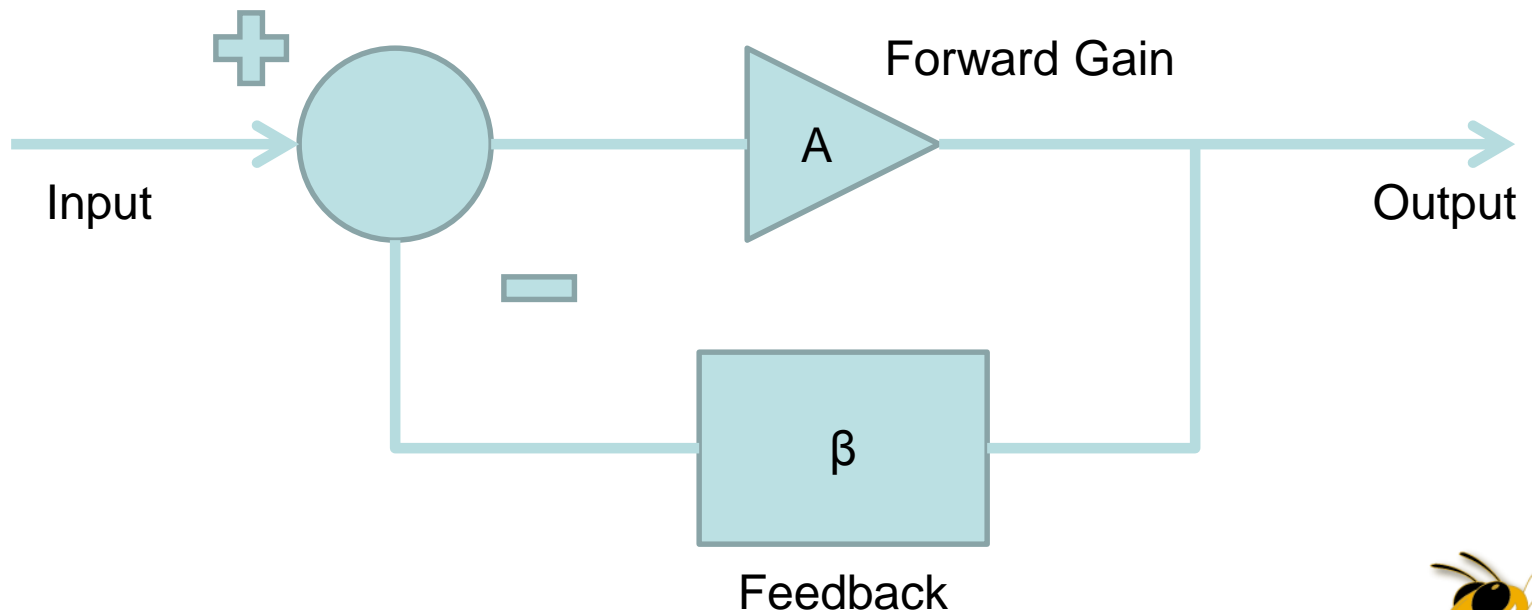
- Before the Op-Amp: Harold S. Black develops the feedback amplifier for the Western Electric Company (1920-1930)



History of the Op-Amp – The Dawn

- **The Vacuum Tube Age**

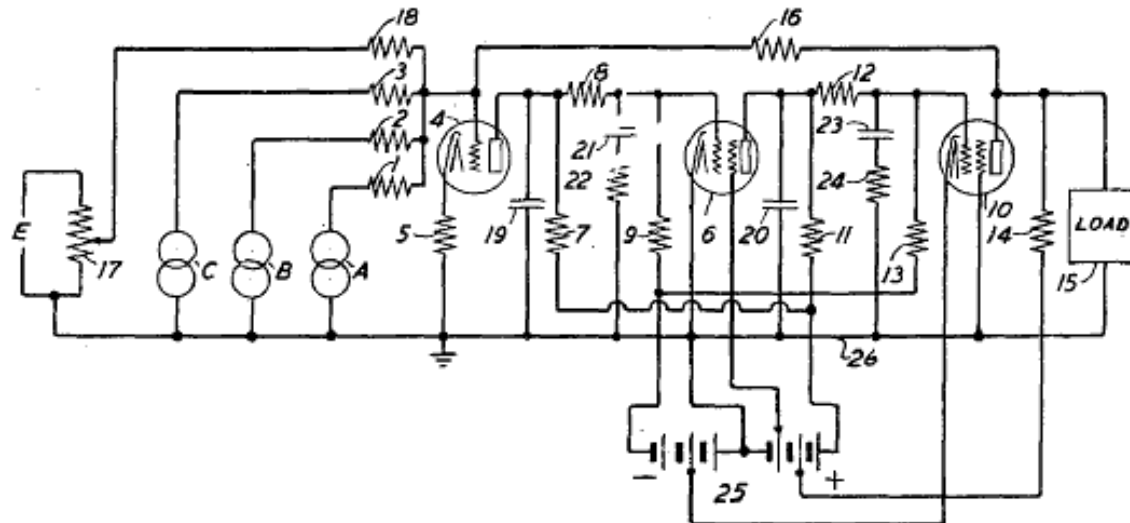- The First Op-Amp: (1930 – 1940) Designed by Karl Swartzel for the Bell Labs M9 gun director
- Uses 3 vacuum tubes, only one input, and ± 350 V to attain a gain of 90 dB
- Loebe Julie then develops an Op-Amp with two inputs: Inverting and Non-inverting



History of the Op-Amp – The Shift

- The end of Vacuum Tubes was built up during the 1950's-1960's to the advent of solid-state electronics

1. The Transistor
2. The Integrated Circuit
3. The Planar Process



History of the Op-Amp – The Shift

- 1960s: beginning of the Solid State Op-Amp
- Example: GAP/R P45 (1961 – 1971)
 - Runs on ± 15 V, but costs \$118 for 1 – 4
- The GAP/R PP65 (1962) makes the Op-Amp into a circuit component as a potted module



Mathematics of the Op-Amp

- The gain of the Op-Amp itself is calculated as:

$$G = V_{\text{out}} / (V_{+} - V_{-})$$


- The maximum output is the power supply voltage
- When used in a circuit, the gain of the circuit (as opposed to the op-amp component) is:

$$A_v = V_{\text{out}} / V_{\text{in}}$$




Op-Amp Saturation

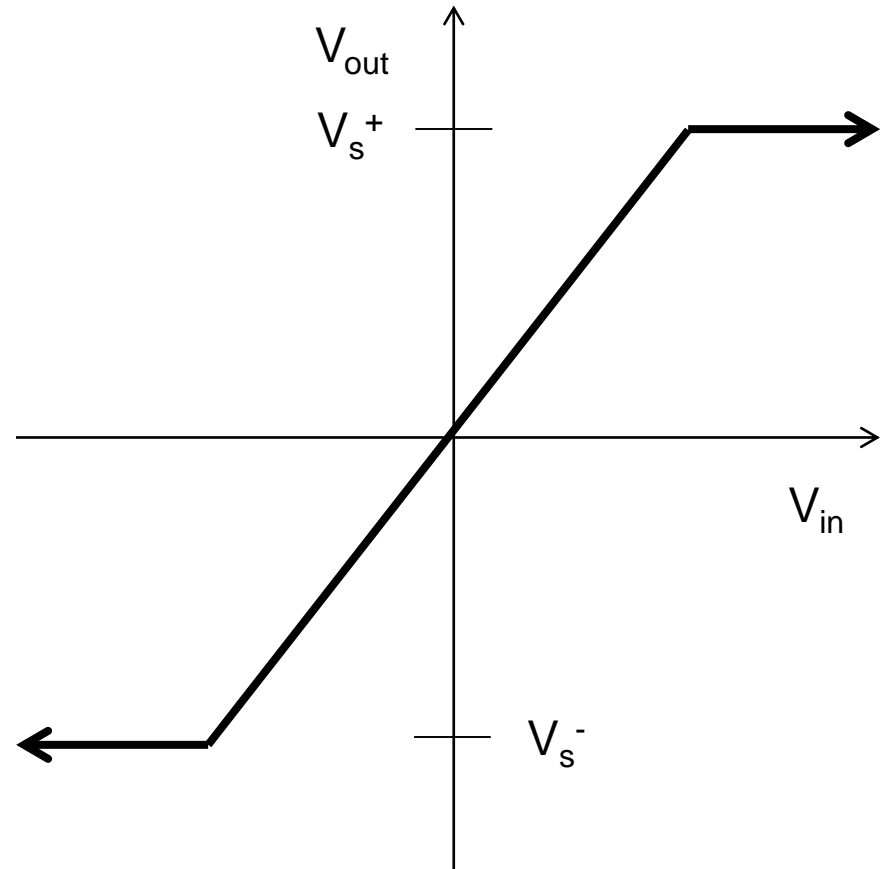
- As mentioned earlier, the maximum output value is the **supply voltage**, positive and negative.
- The gain (G) is the slope between saturation points.



741 Op-Amp Schematic

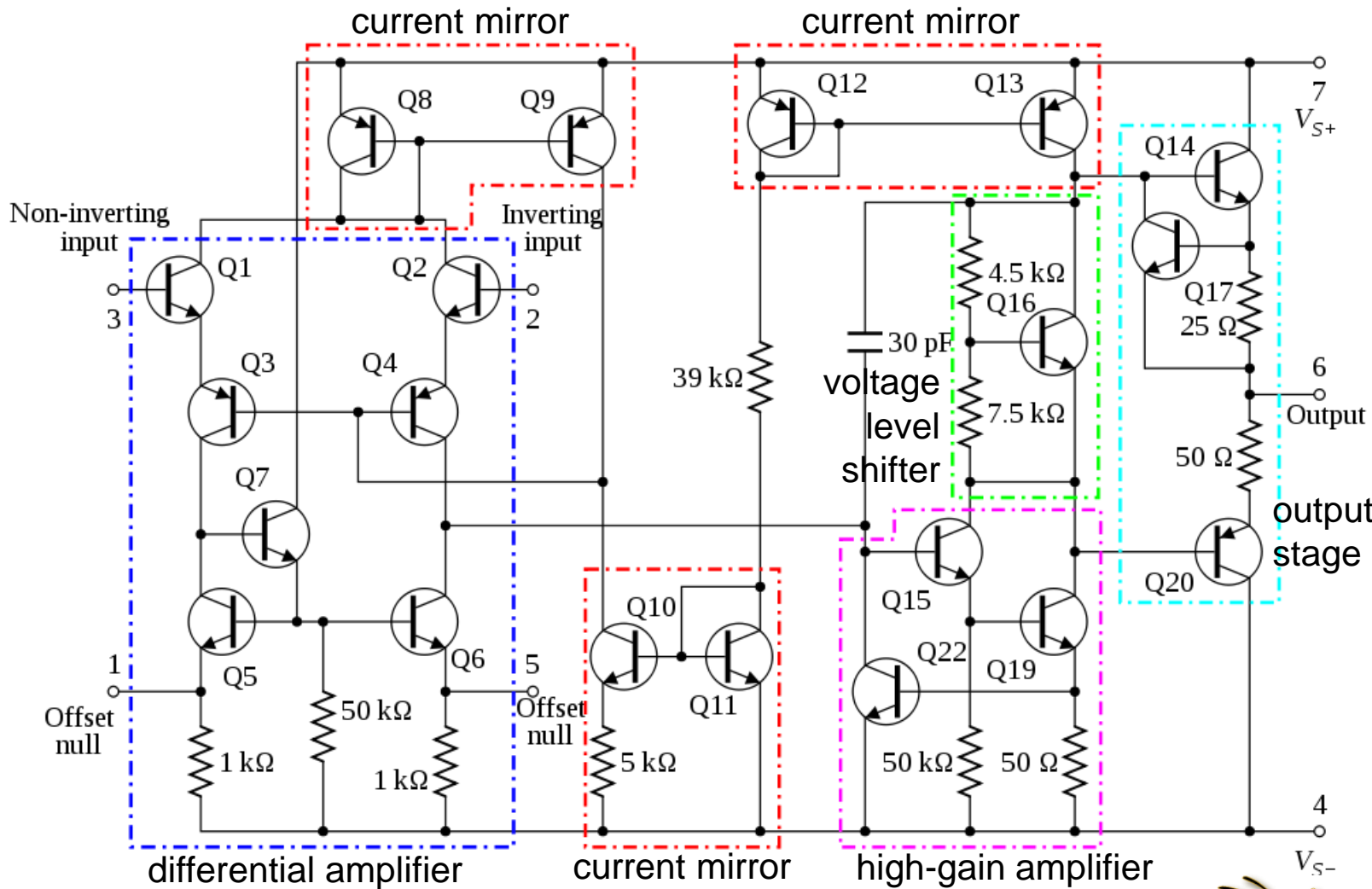


Op-Amp Characteristics

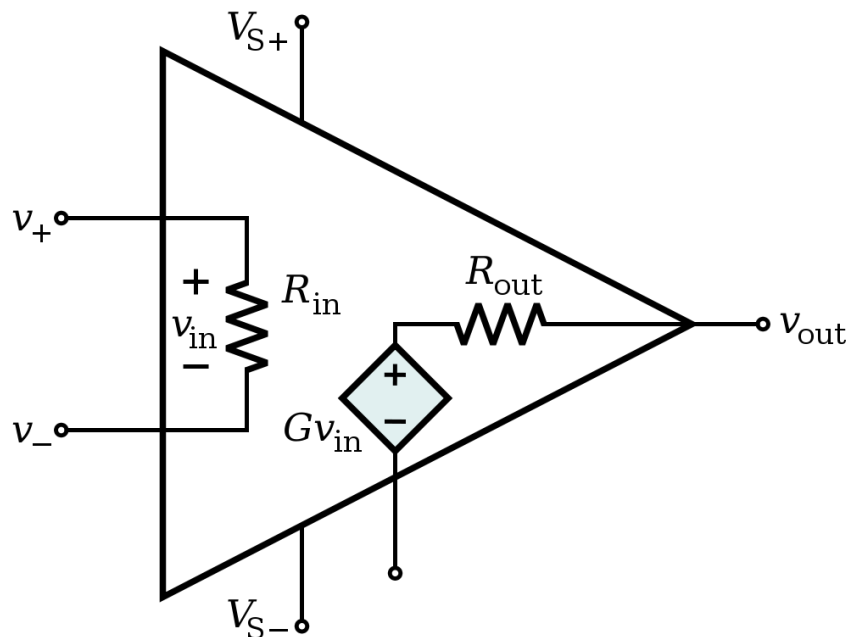

- Open-loop gain G is typically over 9000
 - But closed-loop gain is much smaller
- R_{in} is very large ($M\Omega$ or larger)
- R_{out} is small (75Ω or smaller)
 - Effective output impedance in closed loop is very small




Ideal Op-Amp Characteristics

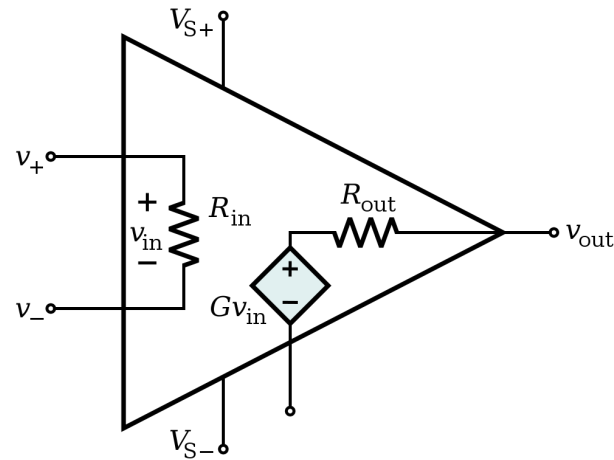

- Open-loop gain G is infinite
- R_{in} is infinite
 - Zero input current
- R_{out} is zero



Ideal Op-Amp Analysis

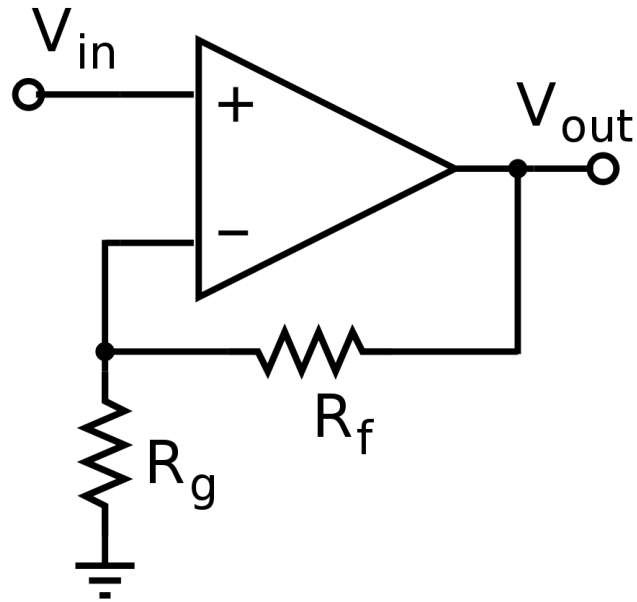


To analyze an op-amp feedback circuit:

- Assume no current flows into either input terminal
- Assume no current flows out of the output terminal
- Constrain: $V_+ = V_-$




Inverting Amplifier Analysis

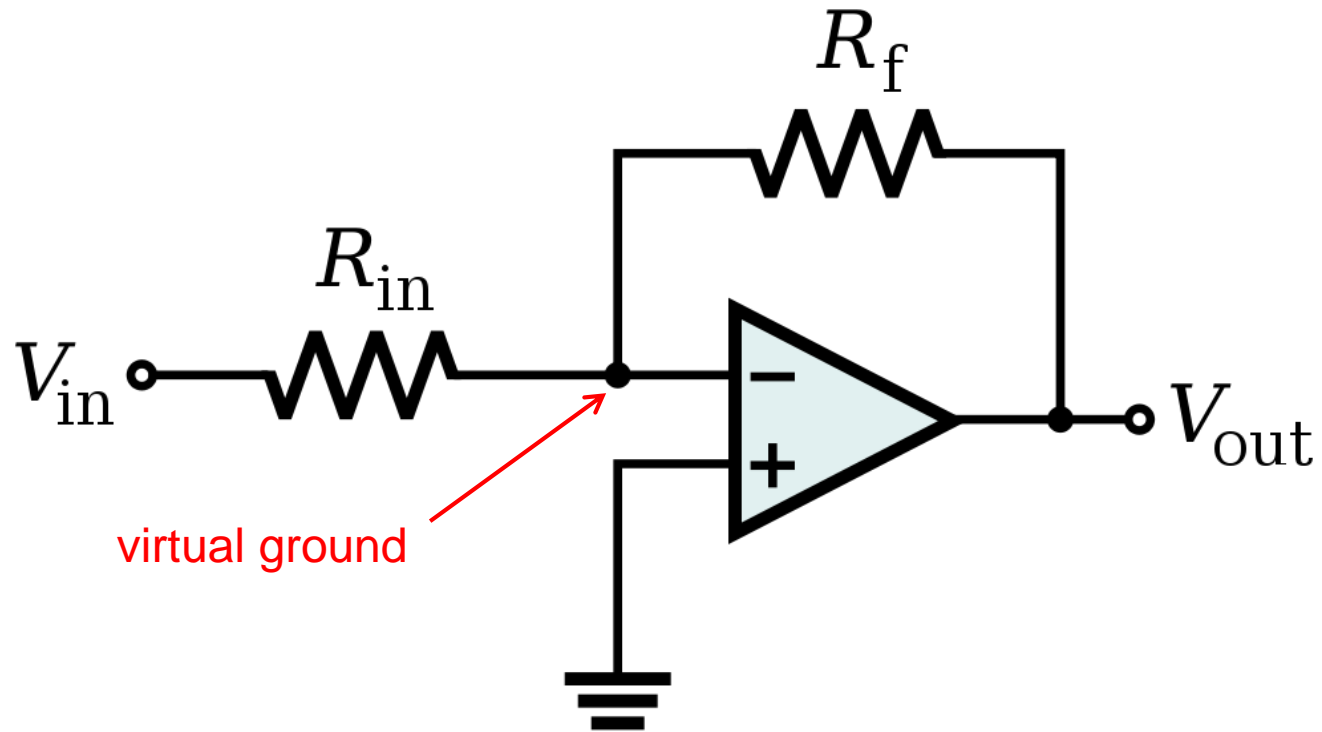

$$V_{out} = -\frac{R_f}{R_{in}} V_{in}$$




Non-Inverting Amplifier Analysis

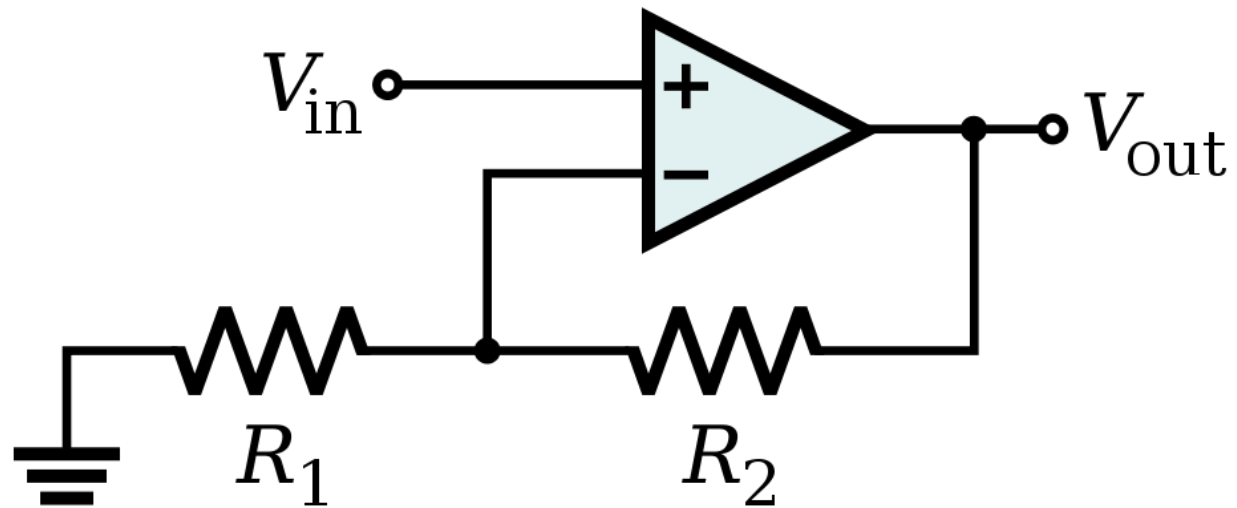


$$V_{out} = V_{in} \left(1 + \frac{R_2}{R_1} \right)$$




Op-Amp Buffer

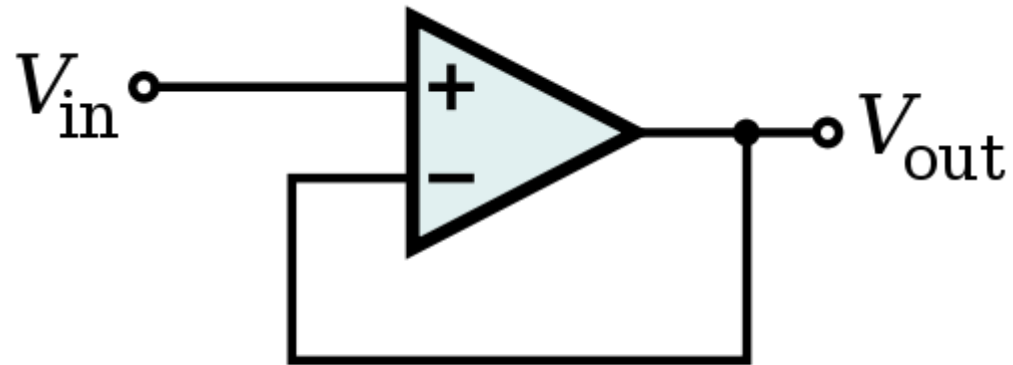

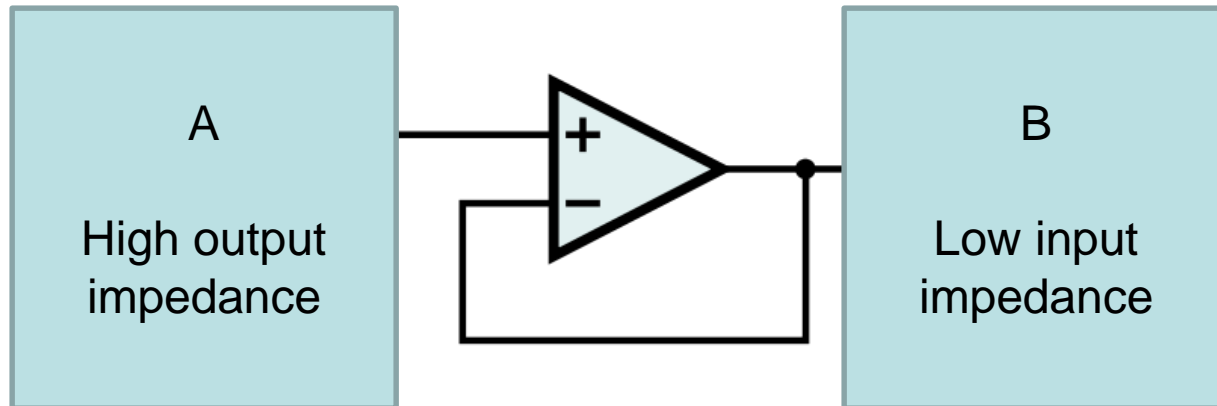$V_{out} = V_{in}$
Isolates loading effects




Op-Amp Differentiator

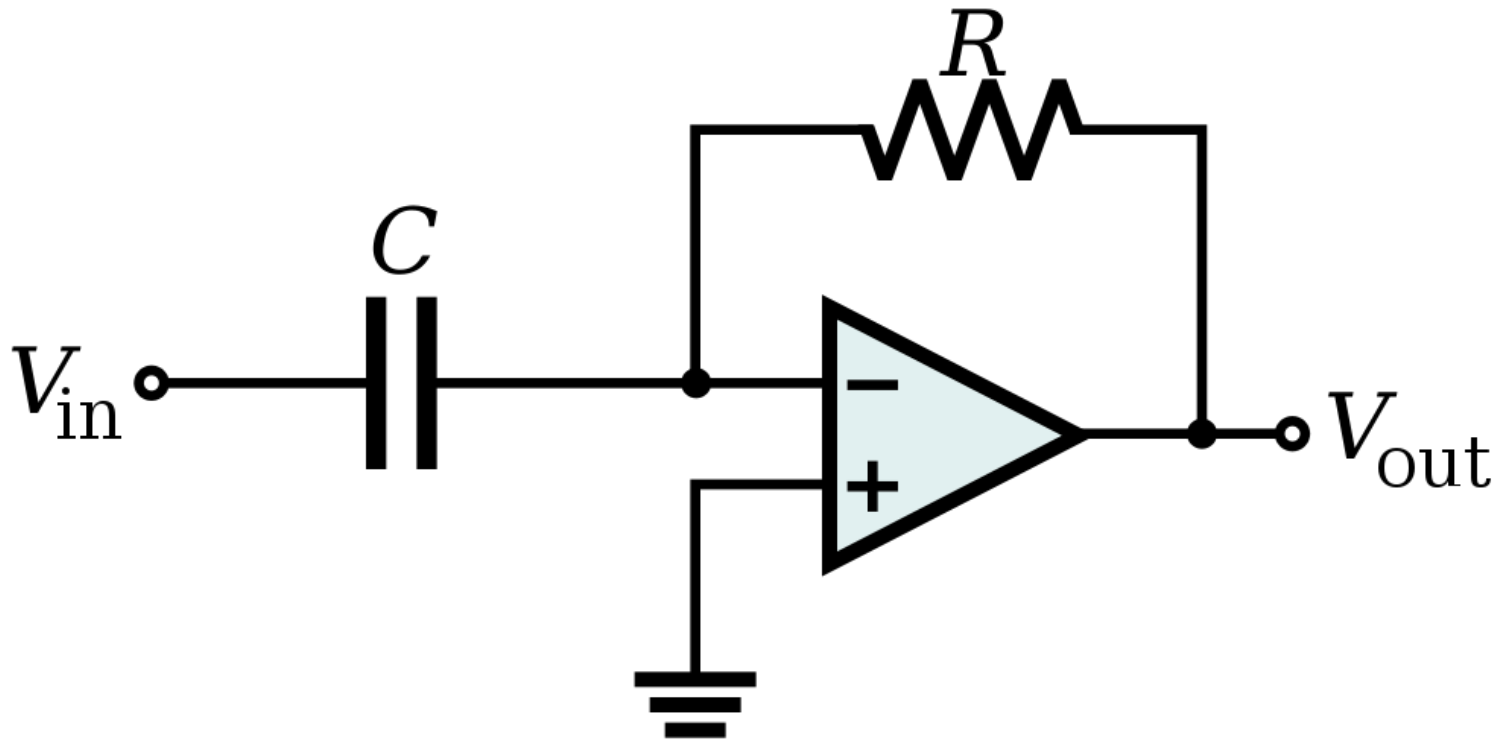

$$V_{out} = -RC \frac{dV_{in}}{dt}$$




Op-Amp Integrator

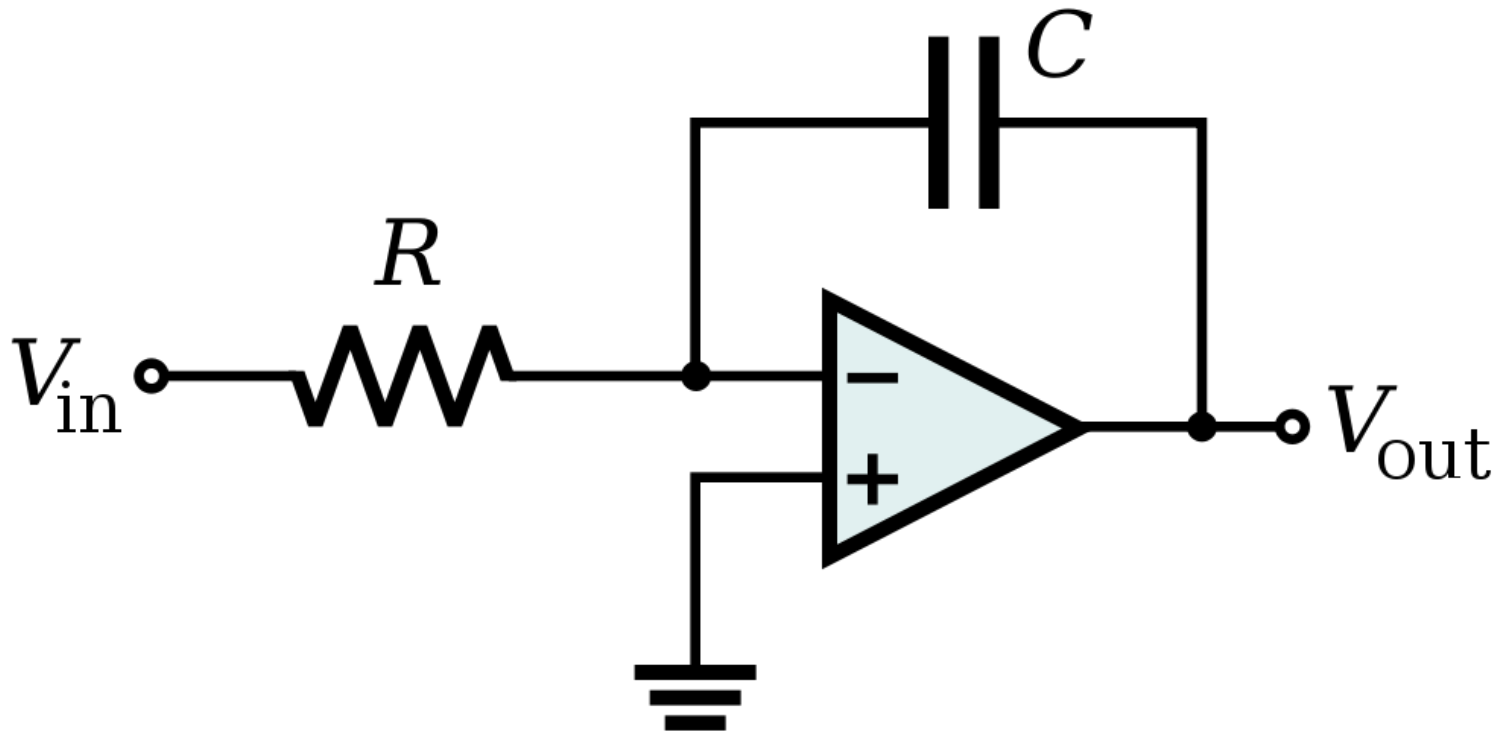

$$V_{out} = - \int_0^t \frac{V_{in}}{RC} dt + V_{initial}$$




Op-Amp Summing Amplifier

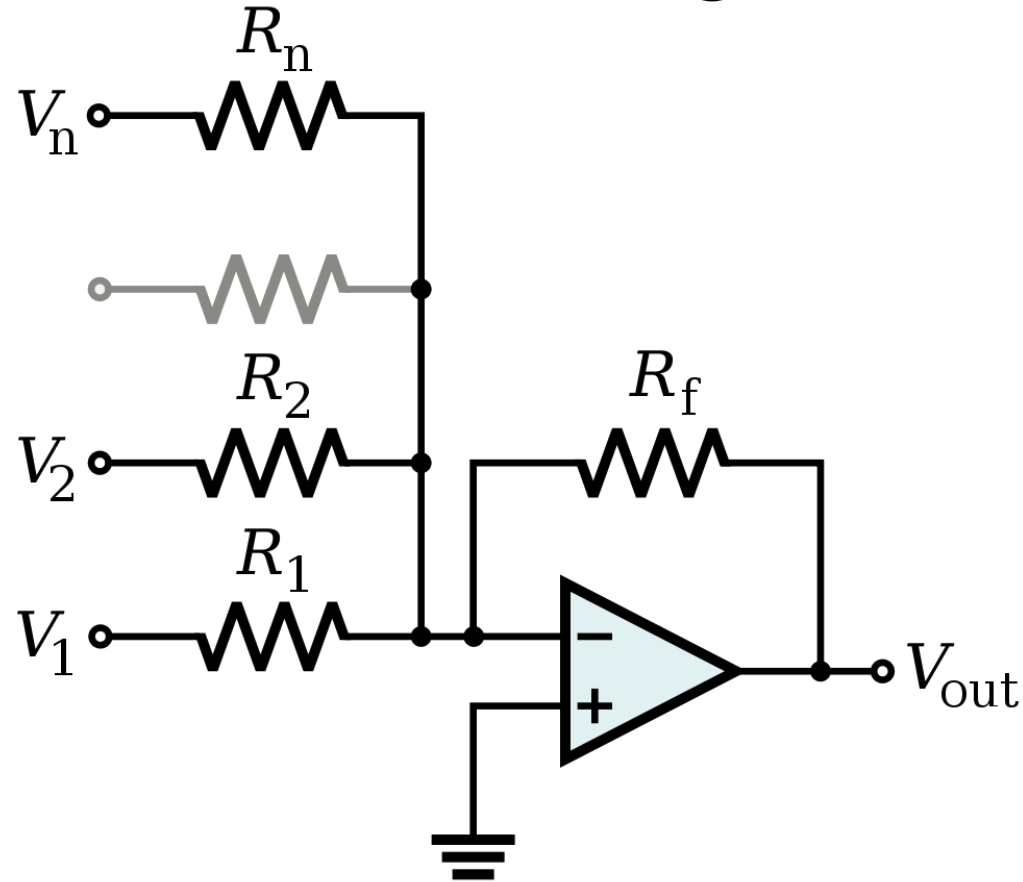

$$V_{out} = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$



Op-Amp Differential Amplifier

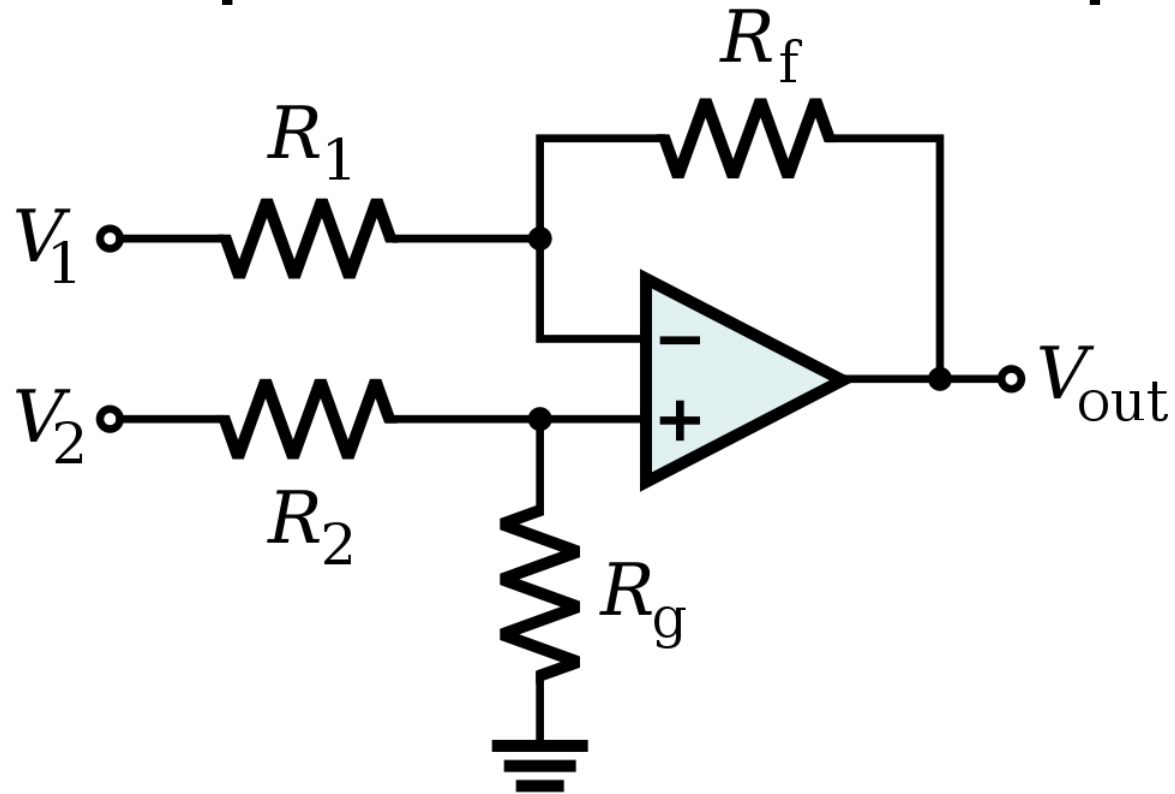

$$V_{out} = \frac{(R_f + R_1) R_g}{(R_g + R_2) R_1} V_2 - \frac{R_f}{R_1} V_1$$

If $R_1 = R_2$ and $R_f = R_g$:
$$V_{out} = \frac{R_f}{R_1} (V_2 - V_1)$$



Applications of Op-Amps

Filters

Types:

- Low pass filter
- High pass filter
- Band pass filter
- Cascading (2 or more filters connected together)


Low pass filter transfer function →

$$H(s) = \frac{-R_2 \omega_c}{sR_1 + R_1 \omega_c}$$

Low pass filter Cutoff frequency →



$$\omega_c = \frac{1}{R_2 C}$$

Low pass filter

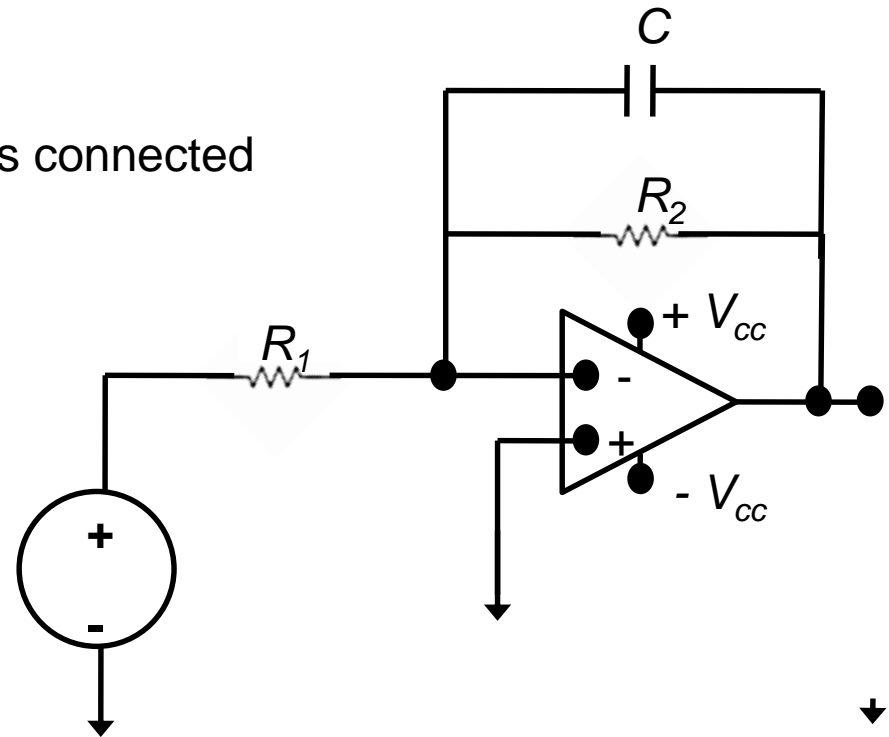


Applications of Op-Amps

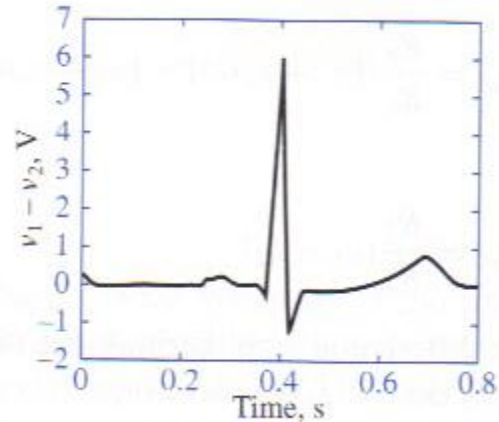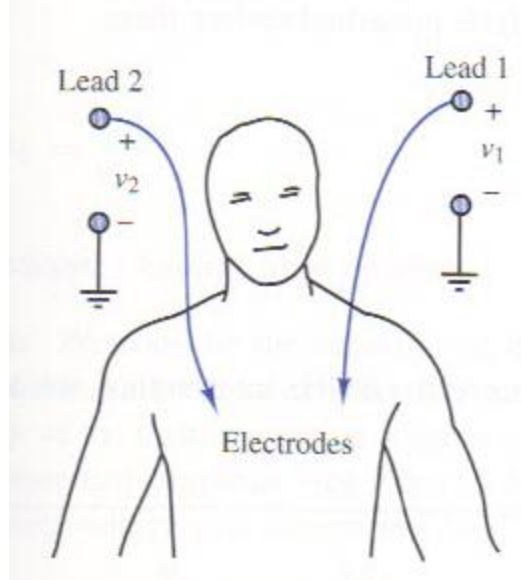- Electrocardiogram (EKG) Amplification
 - Need to measure difference in voltage from lead 1 and lead 2
 - 60 Hz interference from electrical equipment




Applications of Op-Amps

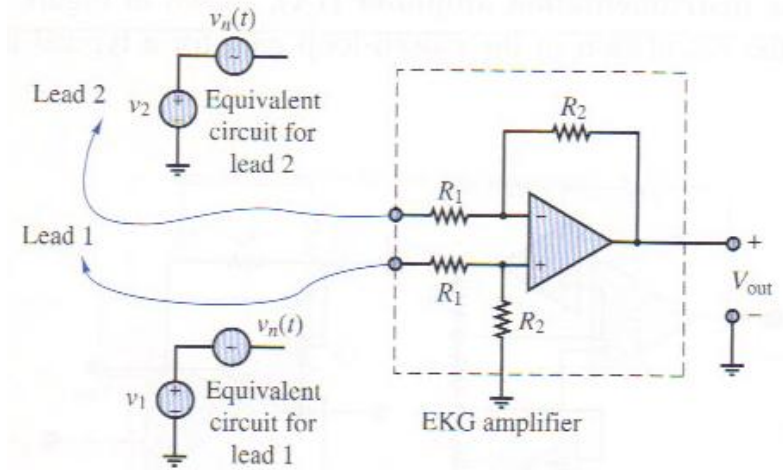- Simple EKG circuit
 - Uses differential amplifier to cancel common mode signal and amplify differential mode signal





- Realistic EKG circuit
 - Uses two non-inverting amplifiers to first amplify voltage from each lead, followed by differential amplifier
 - Forms an “instrumentation amplifier”



Non-inverting Amplifier

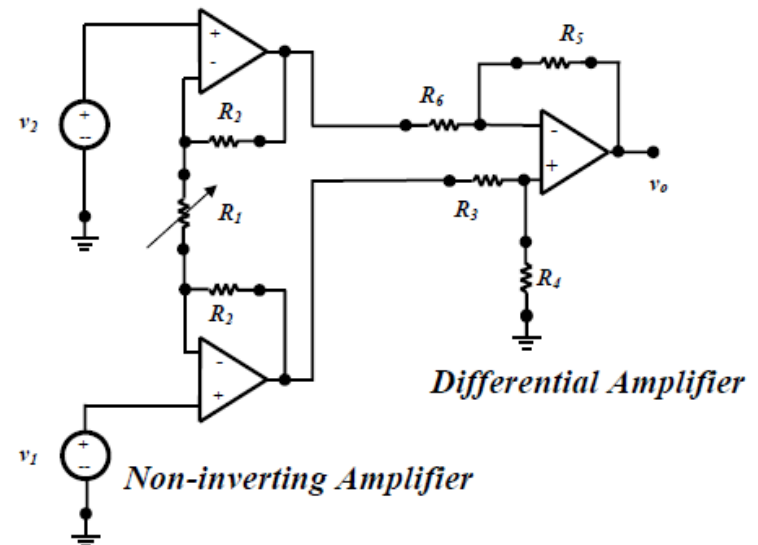

Strain Gauge

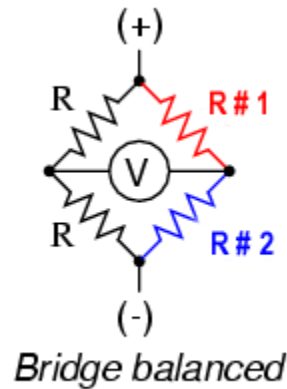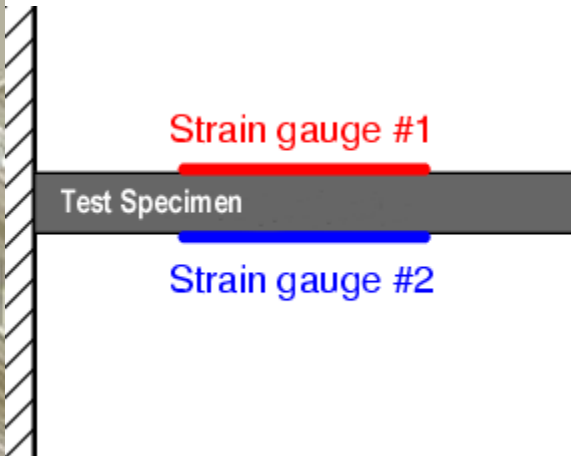

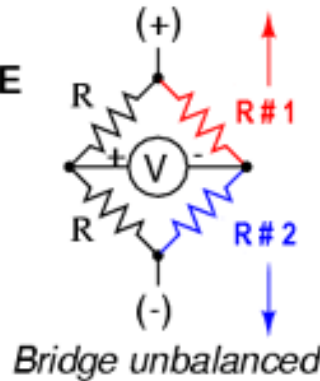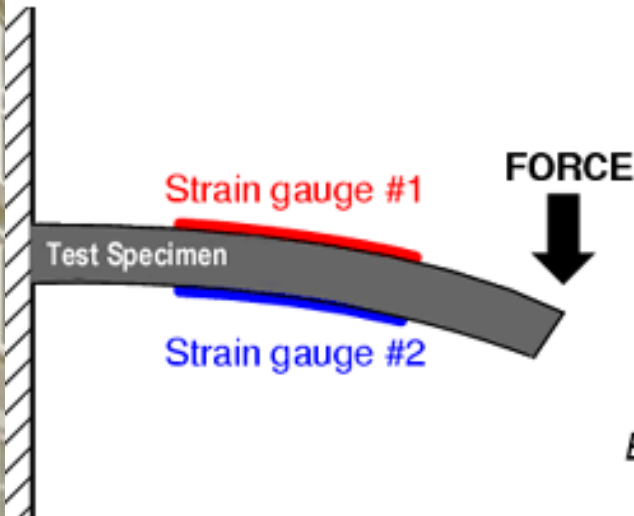Use a Wheatstone bridge to determine the strain of an element by measuring the change in resistance of a strain gauge



(No strain) Balanced Bridge

$$R \#1 = R \#2$$

(Strain) Unbalanced Bridge


$$R \#1 \neq R \#2$$



Strain Gauge

Half-Bridge Arrangement

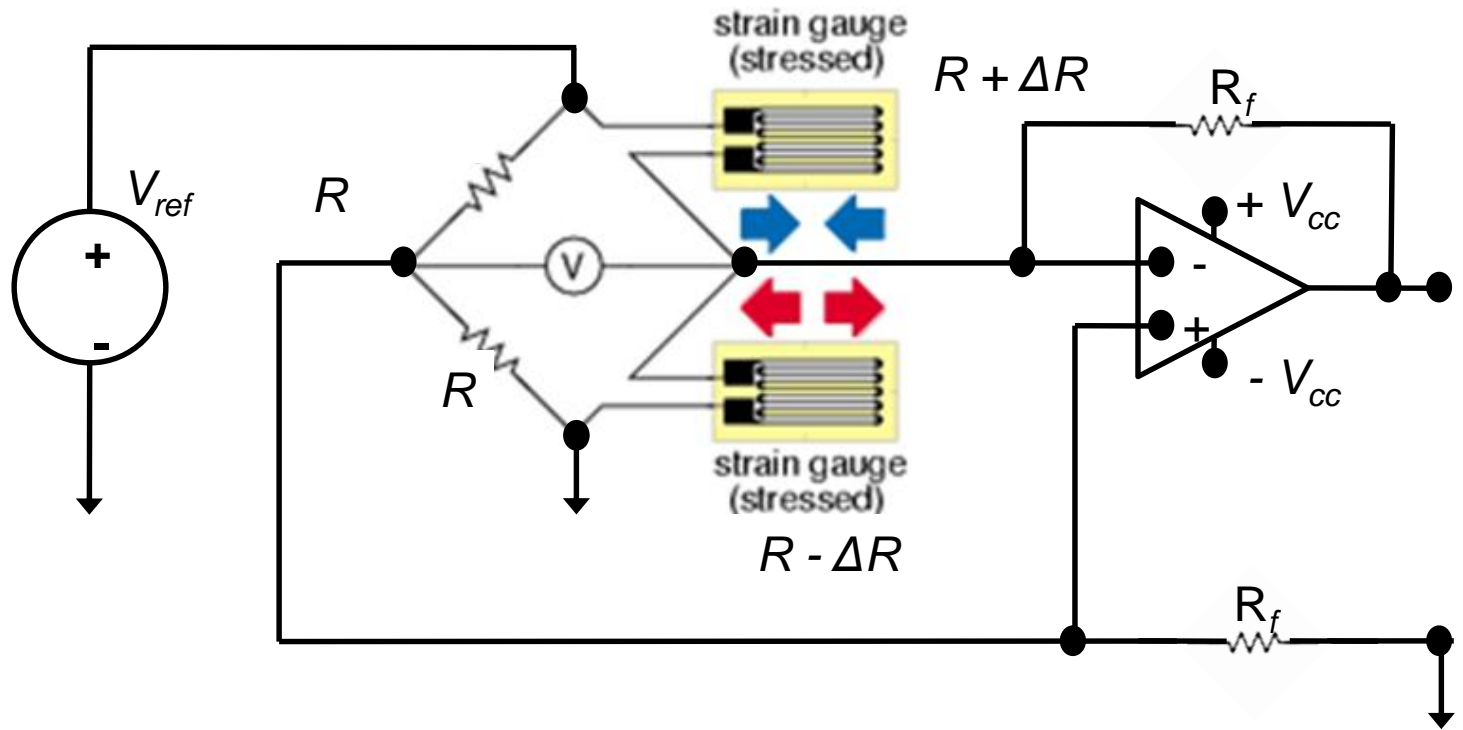Op amp used to amplify output from strain gauge





Using KCL at the inverting and non-inverting terminals of the op amp we find that \rightarrow

$$\epsilon \sim V_o = 2\Delta R(R_f/R^2)$$




Applications of Op-Amps

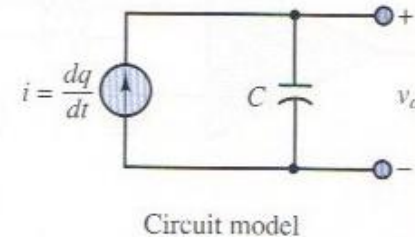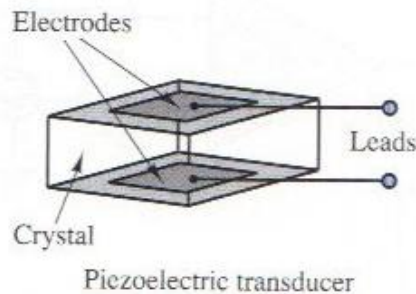
- Piezoelectric Transducer
 - Used to measure force, pressure, acceleration
 - Piezoelectric crystal generates an electric charge in response to deformation



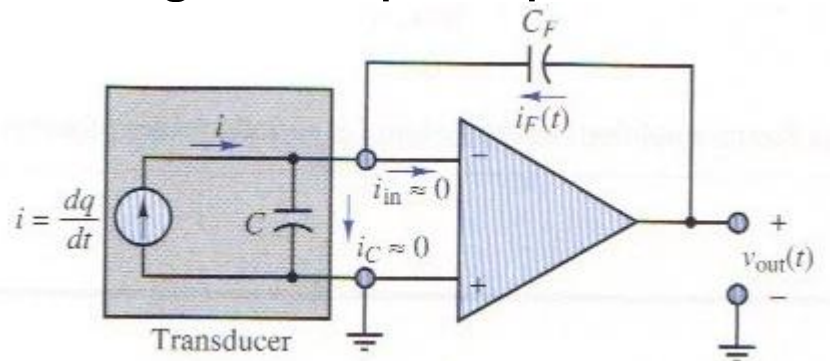- Use Charge Amplifier
 - Just an integrator op-amp circuit



PID Controller – System Block Diagram

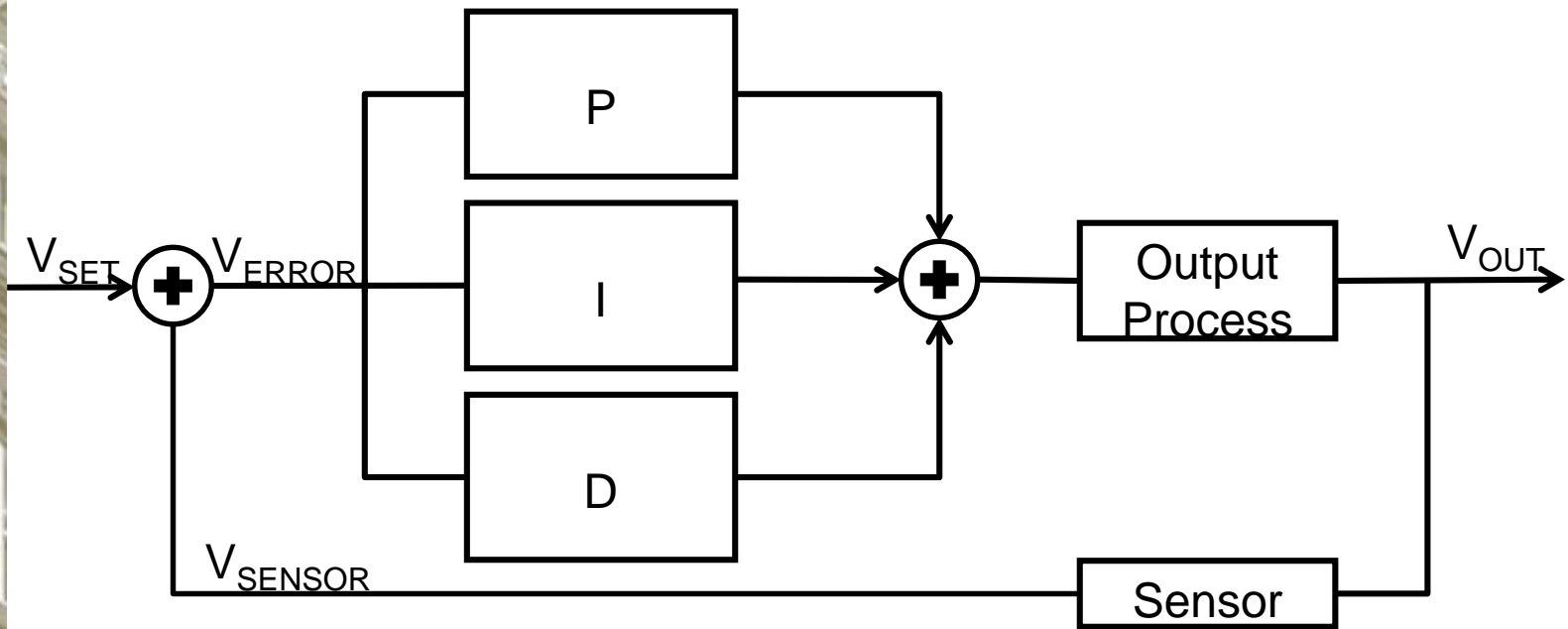


- Goal is to have $V_{\text{SET}} = V_{\text{OUT}}$
- Remember that $V_{\text{ERROR}} = V_{\text{SET}} - V_{\text{SENSOR}}$
- Output Process uses V_{ERROR} from the PID controller to adjust V_{out} such that it is $\sim V_{\text{SET}}$



Applications

PID Controller – System Circuit Diagram

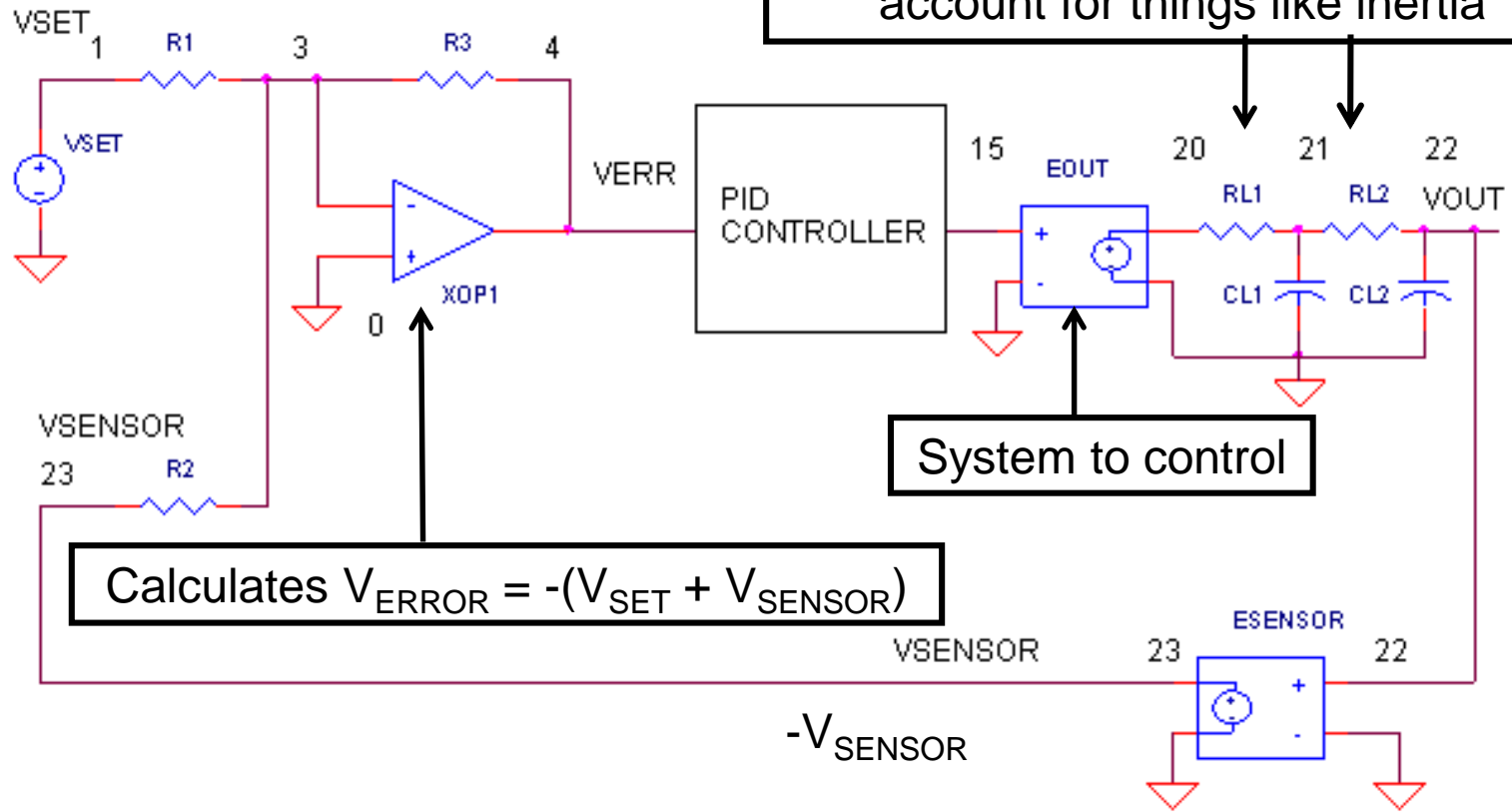Signal conditioning allows you to introduce a time delay which could account for things like inertia




Source:

http://www.ecircuitcenter.com/Circuits/op_pid/op_pid.htm



Applications

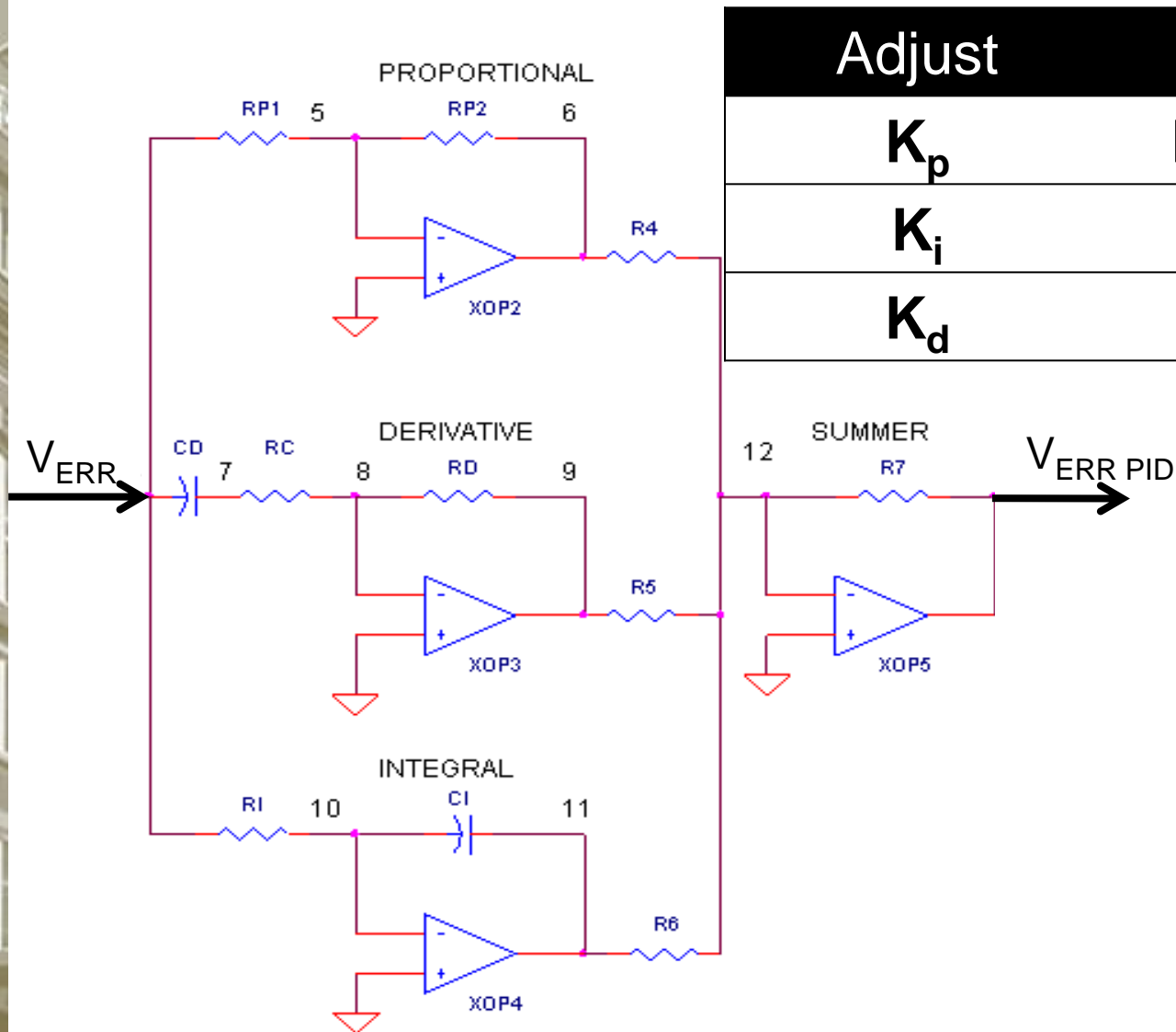PID Controller – PID Controller Circuit Diagram




Adjust	Change
K_p	$RP1, RP2$
K_i	RI, CI
K_d	RD, CD




Applications of Op-Amps

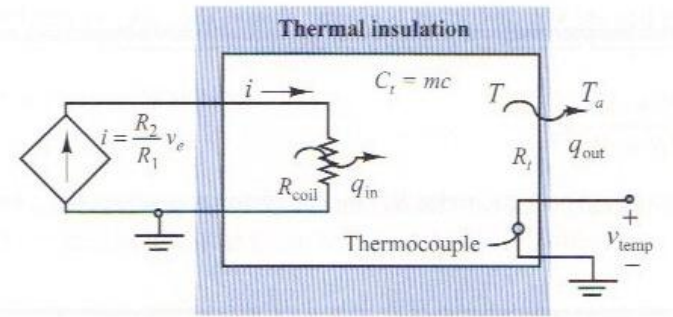- Example of PI Control: Temperature Control

- Thermal System we wish to automatically control the temperature of:




- Block Diagram of Control System:

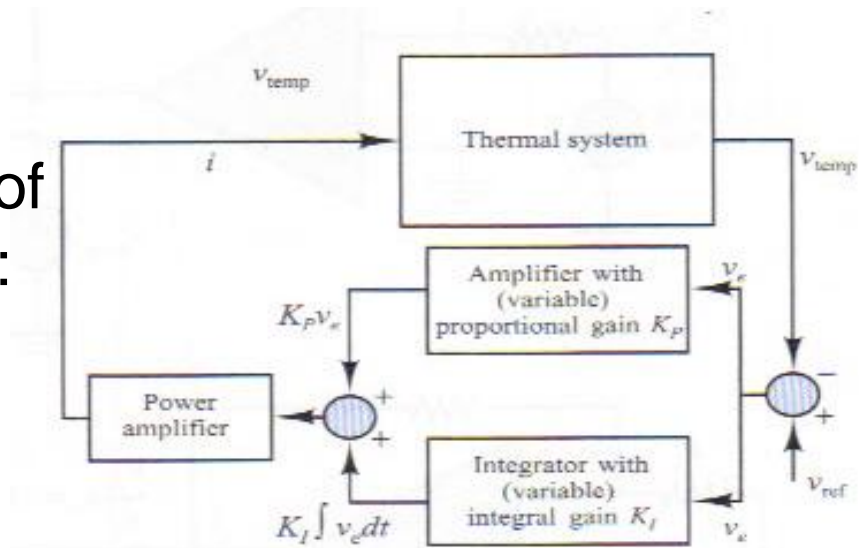

Applications of Op-Amps

- Example of PI Control: Temperature Control

- Voltage Error Circuit:

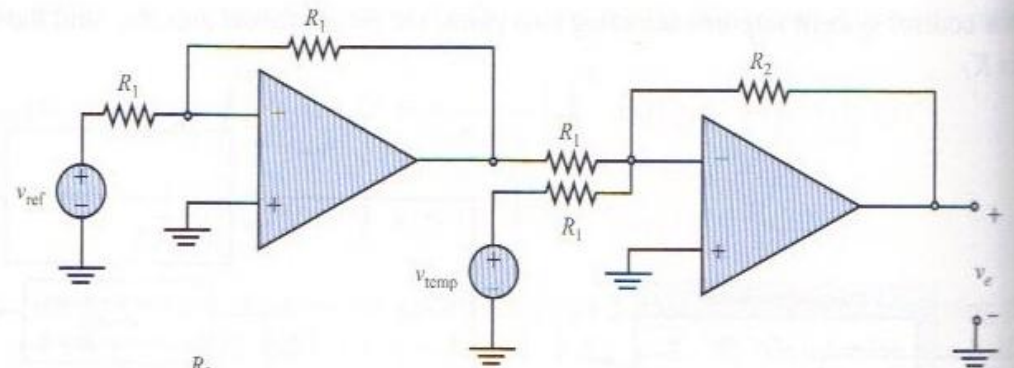

- Proportional-Integral Control Circuit:

